

Modeling Sequential Circuits and FSMs with Verilog

Prof. Chien-Nan Liu
TEL: 03-4227151 ext:34534
Email: jimmy@ee.ncu.edu.tw

5-1

Sequential Circuit Design

- Typical design procedure
 1. Obtain either the state diagram or the state table from the statement of the problem
 2. Reduce the number of states if necessary
 3. Assign binary codes to the states
 4. Obtain the binary coded state table
 5. Choose the type of flip-flop to be used
 6. Derive the simplified flip-flop input equations and output equations from the state table
 7. Draw the logic diagram with D flip-flops and combinational gates according to those equations


5-2

Build the State Diagram

- Example 4-1:

Implement a circuit that recognizes the occurrence of the sequence of bits **1101** on X by making Z equal to 1 when the previous three inputs to the circuit were 110 and current input is a 1.

- Build the state diagram:

 

5-3

Obtain the State Table

 


TABLE 4-5
State Table for State Diagram in Figure 4-21

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	A	B	0	1


Table 4-5 State Table for State Diagram in Figure 4-21

5-4


Derive the Equations

TABLE 4-8
State Table for Design Example


Present State		Input X	Next State		Output Y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

 

$$D_A = AB + BX$$

 

$$D_B = \bar{A}X + BX + AB\bar{X}$$

 

$$Y = BX$$

5-5

The Final Circuit

 



Fig. 4-25 Logic Diagram for Sequential Circuit with D Flip-Flops

5-6

Designing with Unused States

TABLE 4-9
State Table for Second Design Example

Present State			Input	Next State		
A	B	C	X	A	B	C
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	1	0	0
0	1	1	0	0	0	1
0	1	1	1	1	0	0
1	0	0	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	1	0	0

 

Only 5 states are used !!

Unused states are treated as don't cares.

$$D_C = \bar{X}$$

5-7

State Assignment


- State assignment: determine the binary representations of the states in a circuit
- For a circuit with n state registers, there are 2^n possible state assignments
- State assignments have large impacts on the resultant circuit area, performance, ...
- Many coding methods exist
 - One-hot: n bits for n states (one-to-one mapping)
 - Gray code: change only one bit between adjacent states
 - Minimum length encoding: require $(n^{1/2} + 1)$ registers
 - Ad-hoc: determine by experience
- Some general guidelines can be referenced

5-8


Guidelines for State Assignment

- Assignments for two states are adjacent if they differ in only one variable
 - 010 and 011 are adjacent
 - 010 and 001 are not adjacent
- Guideline 1:** states which have the *same next state* for a *given input* could be given adjacent assignments
- Guideline 2:** states which are *the next states of the same state* could be given adjacent assignments
- Guideline 3:** states which have the *same output* for a *given input* could be given adjacent assignments


Guideline 1

 

Guideline 2

 

Guideline 3


 


5-9

State Assignment Example


- Guideline 1: (S₀,S₁,S₃,S₅) (S₃,S₅) (S₄,S₆) (S₀,S₂,S₄,S₆)
- Guideline 2: (S₁, S₂) (S₂,S₃) (S₁,S₄) (S₂,S₅)X₂ (S₁,S₆)X₂
- Try to fulfill as many of these adjacency conditions as possible
 - It's hard to satisfy all those conditions
 - The conditions that appear more times have higher priority
 - K-map can help us to check those conditions
- Two possible state assignments are demonstrated

ABC	X=0	1	0	1
000	S ₀	S ₁ S ₂	0	0
110	S ₁	S ₃ S ₂	0	0
001	S ₂	S ₁ S ₄	0	0
111	S ₃	S ₅ S ₂	0	0
011	S ₄	S ₁ S ₆	0	0
101	S ₅	S ₅ S ₂	1	0
010	S ₆	S ₁ S ₆	0	1

  


5-10

Effects of the Guidelines

 

(a) Next state maps for Fig. 15-14

 

(b) Next state maps for Fig. 15-14 (cont.)


5-11

Finite State Machine

- FSM: Finite State Machine
 - Sequential circuits with “finite” states
 - Most sequential circuits can be classified as FSMs
- Two primary categories:
 - Mealy machine
 - Outputs depend on current states and inputs
 - Moore machine
 - Outputs depend on current states only


5-12

FSM Structures (1/3)

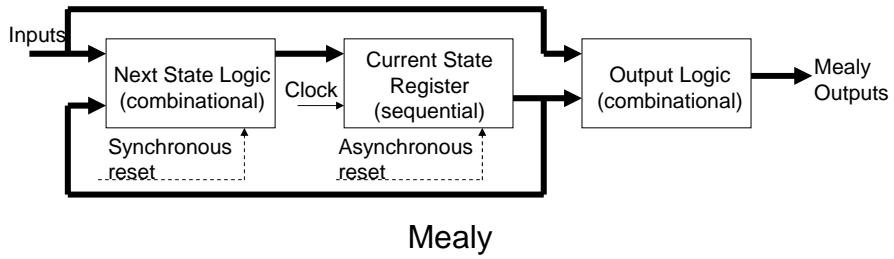


5-13

FSM Structures (2/3)

 

5-14


FSM Structures (3/3)

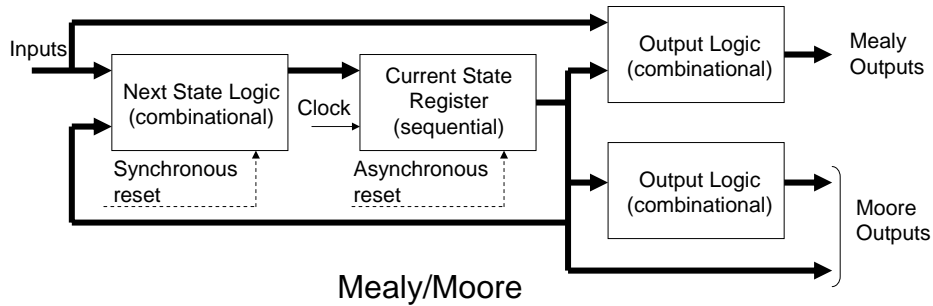

5-15

Coding for FSM

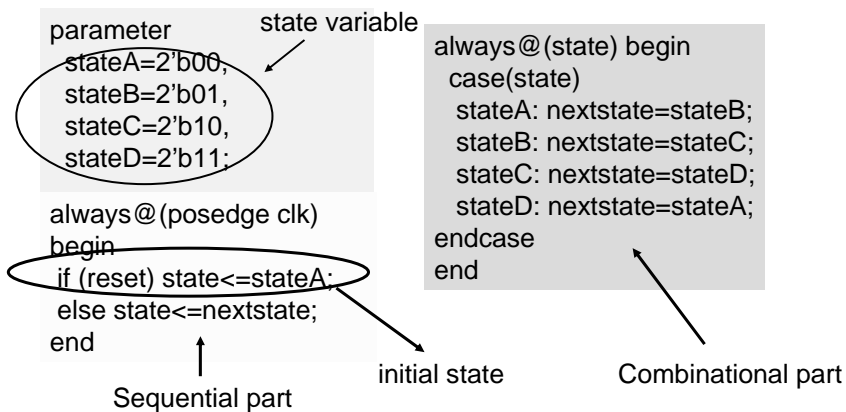- Separate the combination part and the sequential part
- Use parameters to define the state variables



5-16


Blocking v.s Non-Blocking

- Use non-blocking assignments for sequential block
 - Store values until the end of the time slice
 - Avoid simulation race conditions or ambiguity of results
- Use blocking assignments for combinational block
 - Blocking assignments occur immediate in nature

5-17

Blocking Assignment
 
```
always @(posedge clk)
begin
  outa=in;
  outb=outa;
  outc=outb;
end
```



5-18

Non-Blocking Assignment

```

always @(posedge clk)
begin
  outa<=in;
  outb<=outa;
  outc<=outb;
end


```

==

```

always @(posedge clk)
  outa=in;
always @(posedge clk)
  outb=outa;
always @(posedge clk)
  outc=outb;

```

 

5-19

Illustration of Execution Order

```


always@(posedge clk)
begin
  out1 = 3; ③
end

always@(posedge clk)
begin
  out1 = 0; ①
  out1<= 1; ⑤
  out1 = 2; ②
end

always@(out1)
begin
  out2 = ~out2; ④ ⑥
end

```

0	clk	
bxx	out1	
0	out2	
\$end		
#5		
1	clk	①
b00	out1	②
b10	out1	③
b11	out1	④
1	out2	⑤
b01	out1	⑥
0	out2	⑦

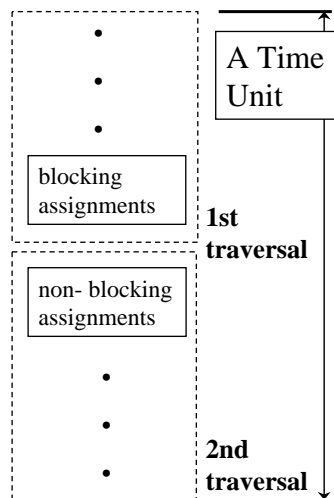

5-20

Example: Sequence Recognizer

```
// Sequence Recognizer: Verilog Process Description
// (See Figure 4-21 for state diagram)
module seq_rec_v(CLK, RESET, X, Z);
  input CLK, RESET, X;
  output Z;
  reg [1:0] state, next_state;
  parameter A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;
  reg Z;
  // state register: implements positive edge-triggered
  // state storage with asynchronous reset.
  always @(posedge CLK or posedge RESET)
  begin
    if (RESET == 1)
      state <= A;
    else
      state <= next_state;
  end
  // next state function: implements next state as function
  // of X and state
  always @(X or state)
  begin
    case (state)
      A: if (X == 1)
          next_state <= B;
        else
          next_state <= A;
      B: if(X) next_state <= C;else next_state <= A;
      C: if(X) next_state <= C;else next_state <= D;
      D: if(X) next_state <= B;else next_state <= A;
    endcase
  end
  // output function: implements output as function
  // of X and state
  always @(X or state)
  begin
    case (state)
      A: Z <= 0;
      B: Z <= 0;
      C: Z <= 0;
      D: Z <= X ? 1 : 0;
    endcase
  end
end
endmodule
```

Just describe
state-by-state !!

5-21

Various Coding Styles for FSM

- There are many different coding styles can be used to describe a FSM
 - HDL is a very flexible language
- Typical coding styles:
 - 1-process FSM
 - 2-process FSM
 - 3-process (or more) FSM

5-22


1-Process FSM

- Lump all descriptions into a single process

```

module counter (clk, rst, load, in, count) ;
input      clk, rst, load ;
input  [7:0] in ;
output [7:0] count ;
reg  [7:0] count ;

 
always @(posedge clk) begin
    if (rst) count = 0 ;
    else if (load) count = in ;
    else if (count == 255) count = 0 ;
    else count = count + 1 ;
end
endmodule
    
```



256 states 66047 transitions

5-23

2-Process FSM (1/5)

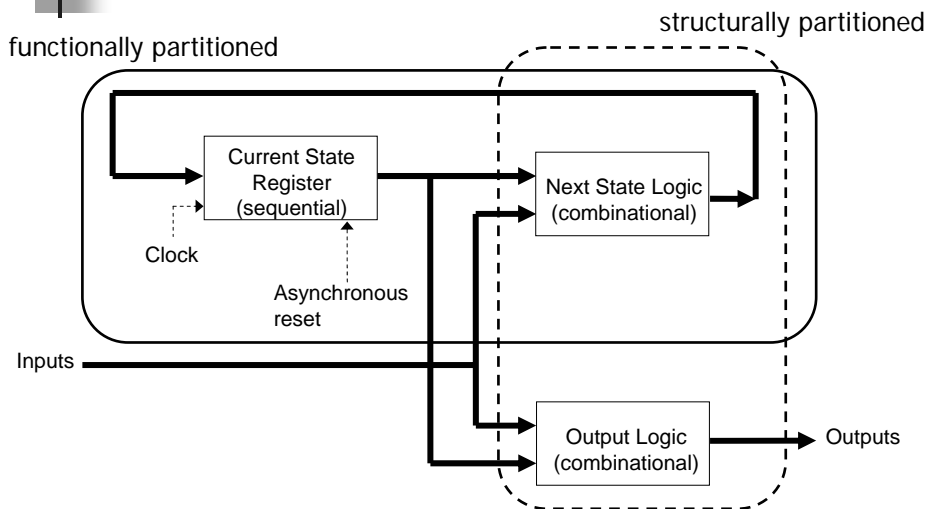

5-24

2-Process FSM (2/5)


```

module FSM_S2 (Clock, Reset, X, Y);
  input Clock, Reset, X;
  output [2:0] Y;
  reg [2:0] Y;
  reg [1:0] CS, NS;
  parameter ST0 = 0, ST1 = 1, ST2 = 2, ST3 = 3;

  always @(X or CS) begin : COMB
    case (CS)
      ST0 : begin
        Y = 1;
        NS = ST1;
      end
      ST1 : begin
        Y = 2;
        if (X) NS = ST3;
        else NS = ST2;
      end
    end
  end

```

2-process,
structurally
partitioned

 

5-25

2-Process FSM (3/5)

```

ST2 : begin
  Y = 3;
  NS = ST3;
end
ST3 : begin
  Y = 4;
  NS = ST0;
end
default : begin
  Y = 1;
  NS = ST0;
end
endcase
end

always @(posedge Clock or posedge Reset)
begin : SEQ
  if (Reset)
    CS <= ST0;
  else
    CS <= NS;
  end
endmodule

```

5-26

2-Process FSM (4/5)

- 2-process, functionally partitioning

```
module FSM_F2 (Clock, Reset, X, Y);
    input  Clock, Reset, X;
    output [2:0] Y;
    reg [2:0] Y;
    reg [1:0] STATE;
    parameter [1:0] ST0 = 0, ST1 = 1, ST2 = 2, ST3 = 3;

    always @(posedge Clock or posedge Reset)
    begin : NEXT_STATE
        if (Reset)
            STATE <= ST0;
        else
```

5-27


2-Process FSM (5/5)

```
        case (STATE)
            ST0 : STATE <= ST1;
            ST1 : begin
                    if (X)
                        STATE <= ST3;
                    else
                        STATE <= ST2;
                end
            ST2 : STATE <= ST3;
            ST3 : STATE <= ST0;
        endcase
    end

        always @(STATE)
        begin : OUT
            case (STATE)
                ST0 : Y = 1;
                ST1 : Y = 2;
                ST2 : Y = 3;
                ST3 : Y = 4;
                default : Y = 1;
            endcase
        end
    endmodule
```

5-28

3-Process FSM (1/4)

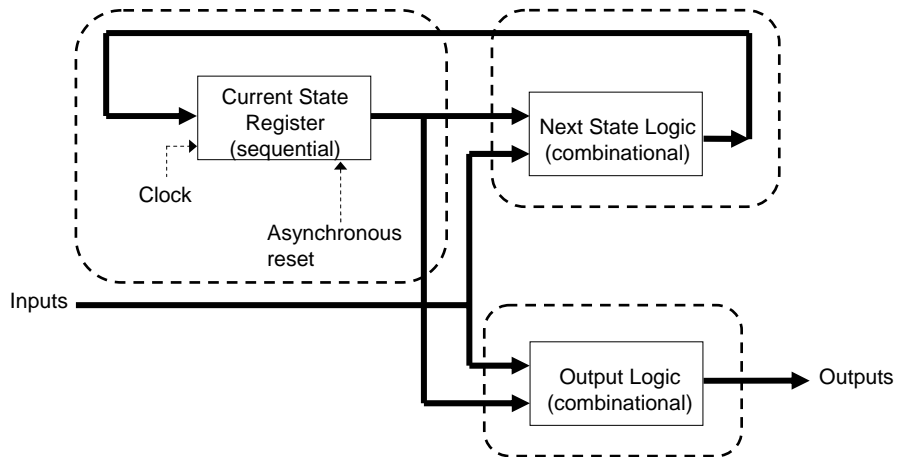

5-29

3-Process FSM (2/4)

- 3-process, structurally partitioning

```
module FSM_S3(Clock, Reset, X, Y);
    input Clock, Reset, X;
    output [2:0] Y;
    reg [2:0] Y;
    reg [1:0] CS, NS;
    parameter [1:0] ST0 = 0, ST1 = 1, ST2 = 2, ST3 = 3;

    always @(X or CS)
    begin : COMB
        NS = ST0;
        case (CS)
```

5-30

3-Process FSM (3/4)

```
ST0 : begin
    NS = ST1;
end
ST1 : begin
    if (X)
        NS = ST3;
    else
        NS = ST2;
    end
end

ST2 : begin
    NS = ST3;
end
ST3 : begin
    NS = ST0;
end
endcase
end
// end process COMB
```

5-31

3-Process FSM (4/4)

```
always @(posedge Clock
        or posedge Reset)
begin : SEQ
    if (Reset)
        CS <= ST0;
    else
        CS <= NS;
    end
end

always @(CS)
begin : OUT
    case (CS)
        ST0 : Y = 1;
        ST1 : Y = 2;
        ST2 : Y = 3;
        ST3 : Y = 4;
        default : Y = 1;
    endcase
end

endmodule
```

5-32