



EECS 150 - Components and Design Techniques for Digital Systems

Lec 26 – CRCs, LFSRs (and a little power)

David Culler

**Electrical Engineering and Computer Sciences
University of California, Berkeley**

<http://www.eecs.berkeley.edu/~culler>
<http://www-inst.eecs.berkeley.edu/~cs150>



Review

- **Concept of error coding**
 - Add a few extra bits (enlarges the space of values) that carry information about all the bits
 - Detect: Simple function to check of entire data+check received correctly
 - » Small subset of the space of possible values
 - Correct: Algorithm for locating nearest valid symbol
- **Hamming codes**
 - Selective use of parity functions
 - Distance + # bit flips
 - Parity: XOR of the bits => single error detection
 - SECDED
 - » $\text{databits} + p + 1 < 2^p$




Outline

- **Introduce LFSR as fancy counter**
- **Practice of Cyclic Redundancy Checks**
 - Burst errors in networks, disks, etc.
- **Theory of LFSRs**
- **Power**




Linear Feedback Shift Registers (LFSRs)

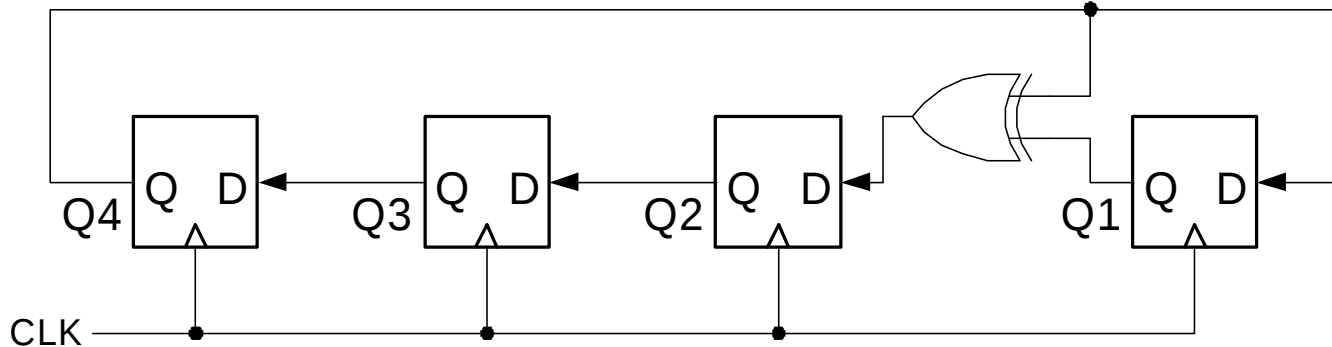- These are n-bit counters exhibiting *pseudo-random* behavior.
- Built from simple shift-registers with a small number of xor gates.
- Used for:
 - random number generation
 - counters
 - error checking and correction
- Advantages:
 - very little hardware
 - high speed operation
- Example 4-bit LFSR:






4-bit LFSR

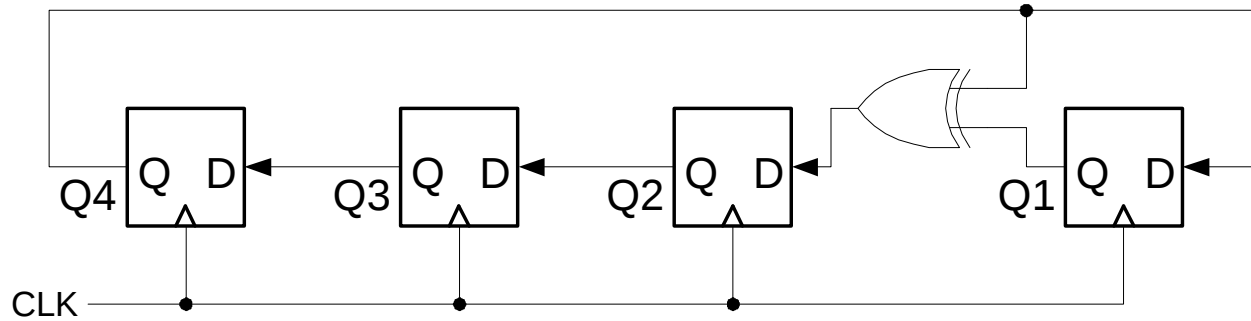

 - Circuit counts through 2^4-1 different non-zero bit patterns.
- Left most bit determines shiftl or more complex operation
- Can build a similar circuit with any number of FFs, may need more xor gates.
- In general, with n flip-flops, 2^{n-1} different non-zero bit patterns.
- (Intuitively, this is a counter that *wraps around* many times and in a strange way.)






Applications of LFSRs


- **Performance:**
 - In general, xors are only ever 2-input and never connect in series.
 - Therefore the minimum clock period for these circuits is:
$$T > T_{2\text{-input-xor}} + \text{clock overhead}$$
 - Very little latency, and independent of n !
- **This can be used as a fast counter, if the particular sequence of count values is not important.**
 - Example: micro-code micro-pc
- **Can be used as a random number generator.**
 - Sequence is a pseudo-random sequence:
 - » numbers appear in a random sequence
 - » repeats every $2^n - 1$ patterns
 - Random numbers useful in:
 - » computer graphics
 - » cryptography
 - » automatic testing
- **Used for error detection and correction**
 - » CRC (cyclic redundancy codes)
 - » ethernet uses them



Concept: Redundant Check

 - Send a message M and a “check” word C
- Simple function on $\langle M, C \rangle$ to determine if both received correctly (with high probability)
- Example: XOR all the bytes in M and append the “checksum” byte, C, at the end
 - Receiver XORs $\langle M, C \rangle$
 - What should result be?
 - What errors are caught?




 


bit i is XOR of ith bit of each byte



Example: TCP Checksum

 




TCP Packet Format

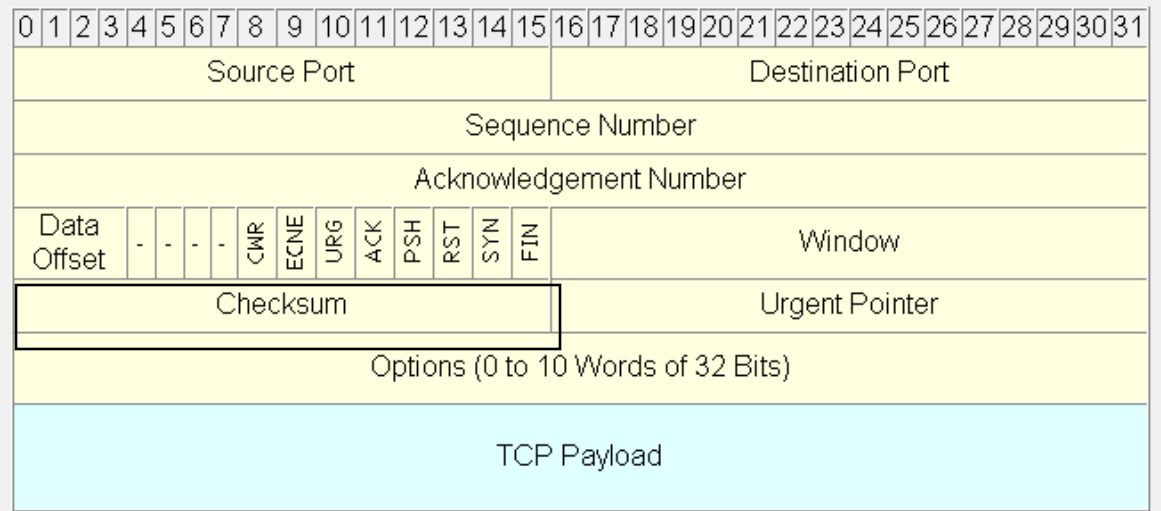

- TCP Checksum a 16-bit **checksum**, consisting of the **one's complement** of the **one's complement sum** of the contents of the TCP segment header and data, is computed by a sender, and included in a segment transmission. **(note end-around carry)**
- Summing all the words, including the checksum word, should yield zero



Example: Ethernet CRC-32

   



CRC concept

- I have a msg polynomial $M(x)$ of degree m
- We both have a generator poly $G(x)$ of degree m
- Let $r(x) = \text{remainder of } M(x) x^n / G(x)$
 - $M(x) x^n = G(x)p(x) + r(x)$
 - $r(x)$ is of degree n
- What is $(M(x) x^n - r(x)) / G(x)$?

n bits of zero at the end
- So I send you $M(x) x^n - r(x)$
 - $m+n$ degree polynomial
 - You divide by $G(x)$ to check
 - $M(x)$ is just the m most significant coefficients, $r(x)$ the lower m

tack on n bits of remainder
Instead of the zeros
- n -bit Message is viewed as coefficients of n -degree polynomial over binary numbers




Announcements

- **Reading**
 - XILINX IEEE 802.3 Cyclic Redundancy Check (pages 1-3)
 - ftp://ftp.rocksoft.com/papers/crc_v3.txt
- **Final on 12/15**
- **What's Going on in EECS?**
 - Towards simulation of a Digital Human
 - Yelick: Simulation of the Human Heart Using the Immersed Boundary Method on Parallel Machines



Digital Human Today: Imaging

 


- **The Visible Human Project**
 - 18,000 digitized sections of the body
 - Male: 1mm sections, released in 1994
 - Female: .33mm sections, released in 1995
 - Goals
 - study of human anatomy
 - testing medical imaging algorithms
 - Current applications:
 - educational, diagnostic, treatment planning, virtual reality, artistic, mathematical and industrial
 - Used by > 1,400 licensees in 42 countries



Image Source: www.madsci.org



THE VISIBLE HUMAN PROJECT®

 



Galois Fields - the theory behind LFSRs

- LFSR circuits performs multiplication on a *field*.
- A field is defined as a set with the following:
 - two operations defined on it:
 - » “addition” and “multiplication”
 - closed under these operations
 - associative and distributive laws hold
 - additive and multiplicative identity elements
 - additive inverse for every element
 - multiplicative inverse for every non-zero element
- Example fields:
 - set of rational numbers
 - set of real numbers
 - set of integers is *not* a field (why?)
- Finite fields are called *Galois* fields.
- Example:
 - Binary numbers 0,1 with XOR as “addition” and AND as “multiplication”.
 - Called GF(2).
 - $0+1 = 1$
 - $1+1 = 0$
 - $0-1 = ?$
 - $1-1 = ?$



Galois Fields - The theory behind LFSRs

- Consider *polynomials* whose coefficients come from GF(2).
- Each term of the form x^n is either present or absent.
- **Examples:** 0 , 1 , x , x^2 , and $x^7 + x^6 + 1$
- With addition and multiplication these form a field:
- “Add”: XOR each element individually with no carry:

$$\begin{array}{r}
 x^4 + x^3 + \quad + x + 1 \\
 + \quad x^4 + \quad + x^2 + x \\
 \hline
 x^3 + x^2 \quad + 1
 \end{array}$$

- “Multiply”: multiplying by x^n is like shifting to the left.

$$\begin{array}{r}
 x^2 + x + 1 \\
 \times \quad \quad x + 1 \\
 \hline
 x^2 + x + 1 \\
 x^3 + x^2 + x \\
 \hline
 x^3 \quad \quad + 1
 \end{array}$$



So what about division (mod)

$$\frac{x^4 + x^2}{x} = x^3 + x \text{ with remainder } 0$$

$$\frac{x^4 + x^2 + 1}{x + 1} = x^3 + x^2 \text{ with remainder } 1$$

$$\begin{array}{r} x^3 + x^2 + 0x + 0 \\ x + 1 \overline{) x^4 + 0x^3 + x^2 + 0x + 1} \\ \underline{x^4 + x^3} \\ x^3 + x^2 \\ \underline{x^3 + x^2} \\ 0x^2 + 0x + 1 \\ \underline{0x + 1} \\ 0 \end{array}$$


Remainder 1



Polynomial division

```


      0 0 0 0 1 0 1
    -----
10011 | 1 0 1 1 0 0 1 0 0 0 0
      1 0 0 1 1
      -----
      0 0 1 0 1
        0 1 0 1 0
          1 0 1 0 1
            -----
            1 0 0 1 1
              0 0 1 0 0
  
```

 

- **When MSB is zero, just shift left, bringing in next bit**
- **When MSB is 1, XOR with divisor and shift!**



CRC encoding

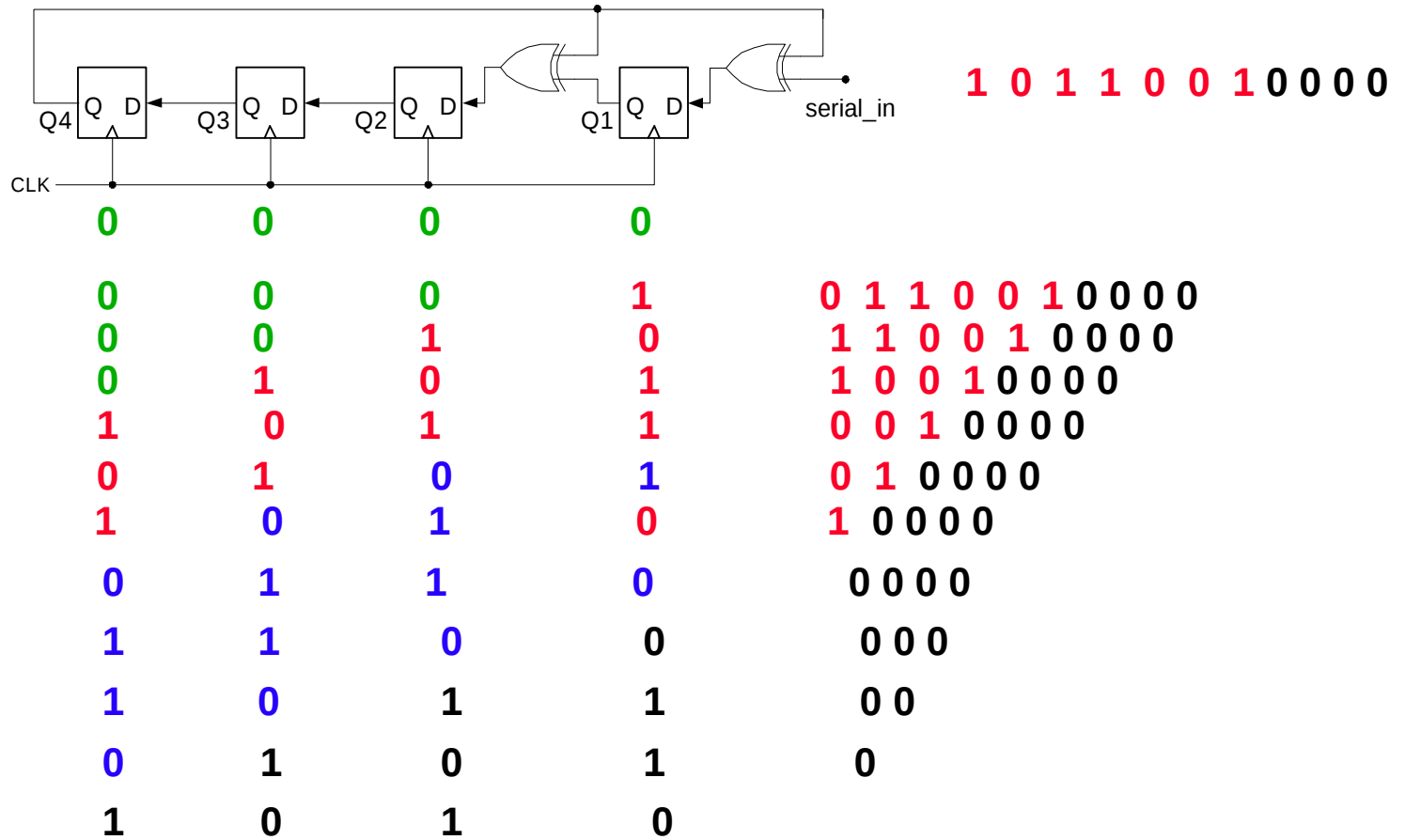


Message sent:

1 0 1 1 0 0 1 1 0 1 0



CRC decoding

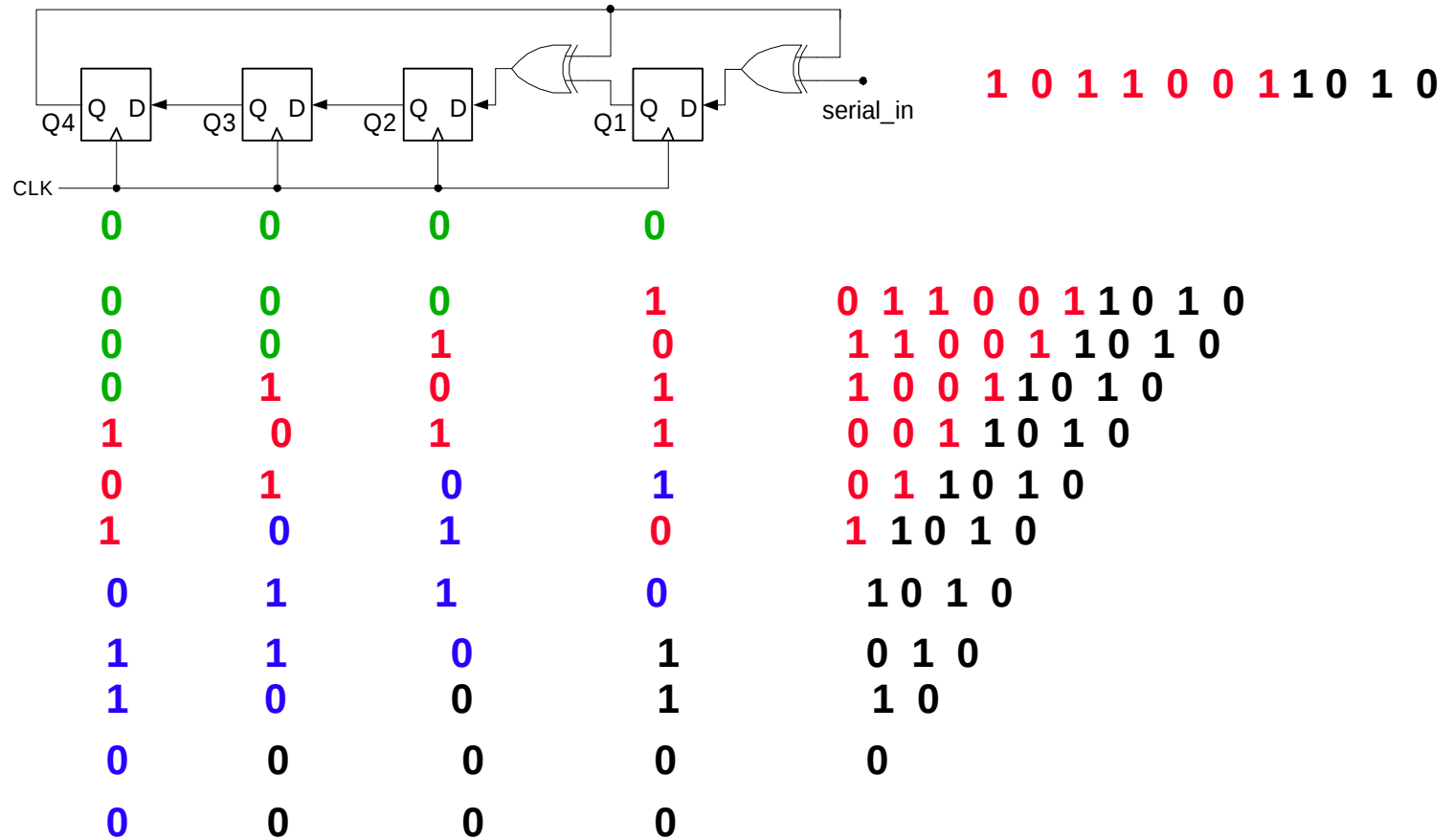



Galois Fields - The theory behind LFSRs

- These polynomials form a *Galois (finite) field* if we take the results of this multiplication modulo a prime polynomial $p(x)$.
 - A prime polynomial is one that cannot be written as the product of two non-trivial polynomials $q(x)r(x)$
 - Perform modulo operation by subtracting a (polynomial) multiple of $p(x)$ from the result. If the multiple is 1, this corresponds to XOR-ing the result with $p(x)$.
- For any degree, there exists at least one prime polynomial.
- With it we can form $GF(2^n)$
- Additionally, ...
- Every Galois field has a primitive element, α , such that all non-zero elements of the field can be expressed as a power of α . By raising α to powers (modulo $p(x)$), all non-zero field elements can be formed.
- Certain choices of $p(x)$ make the simple polynomial x the primitive element. These polynomials are called *primitive*, and one exists for every degree.
- For example, $x^4 + x + 1$ is primitive. So $\alpha = x$ is a primitive element and successive powers of α will generate all non-zero elements of $GF(16)$. *Example on next slide.*



Galois Fields – Primitives

$$\alpha^0 = 1$$

$$\alpha^1 = x$$

$$\alpha^2 = x^2$$

$$\alpha^3 = x^3$$

$$\alpha^4 = x + 1$$

$$\alpha^5 = x^2 + x$$

$$\alpha^6 = x^3 + x^2$$

$$\alpha^7 = x^3 + x + 1$$

$$\alpha^8 = x^2 + 1$$

$$\alpha^9 = x^3 + x$$

$$\alpha^{10} = x^2 + x + 1$$

$$\alpha^{11} = x^3 + x^2 + x$$

$$\alpha^{12} = x^3 + x^2 + x + 1$$

$$\alpha^{13} = x^3 + x^2 + 1$$

$$\alpha^{14} = x^3 + 1$$

$$\alpha^{15} = 1$$

- Note this pattern of coefficients matches the bits from our 4-bit LFSR example.

$$\begin{aligned} \alpha^4 &= x^4 \text{ mod } x^4 + x + 1 \\ &= x^4 \text{ xor } x^4 + x + 1 \\ &= x + 1 \end{aligned}$$

- In general finding primitive polynomials is difficult. Most people just look them up in a table, such as:



Primitive Polynomials

$$x^2 + x + 1$$

$$x^3 + x + 1$$

$$x^4 + x + 1$$

$$x^5 + x^2 + 1$$

$$x^6 + x + 1$$

$$x^7 + x^3 + 1$$

$$x^8 + x^4 + x^3 + x^2 + 1$$

$$x^9 + x^4 + 1$$

$$x^{10} + x^3 + 1$$

$$x^{11} + x^2 + 1$$

$$x^{12} + x^6 + x^4 + x + 1$$

$$x^{13} + x^4 + x^3 + x + 1$$

$$x^{14} + x^{10} + x^6 + x + 1$$

$$x^{15} + x + 1$$

$$x^{16} + x^{12} + x^3 + x + 1$$

$$x^{17} + x^3 + 1$$

$$x^{18} + x^7 + 1$$

$$x^{19} + x^5 + x^2 + x + 1$$

$$x^{20} + x^3 + 1$$

$$x^{21} + x^2 + 1$$

$$x^{22} + x + 1$$

$$x^{23} + x^5 + 1$$

$$x^{24} + x^7 + x^2 + x + 1$$

$$x^{25} + x^3 + 1$$

$$x^{26} + x^6 + x^2 + x + 1$$

$$x^{27} + x^5 + x^2 + x + 1$$

$$x^{28} + x^3 + 1$$

$$x^{29} + x + 1$$

$$x^{30} + x^6 + x^4 + x + 1$$

$$x^{31} + x^3 + 1$$

$$x^{32} + x^7 + x^6 + x^2 + 1$$

Galois Field

Hardware

Multiplication by x

\Leftrightarrow shift left

Taking the result mod $p(x)$

\Leftrightarrow XOR-ing with the coefficients of $p(x)$

when the most significant coefficient is 1.

Obtaining all $2^n - 1$ non-zero \Leftrightarrow Shifting and XOR-ing $2^n - 1$ times.



elements by evaluating x^k

for $k = 1, \dots, 2^n - 1$



Building an LFSR from a Primitive Poly

- For k -bit LFSR number the flip-flops with FF1 on the right.
- The feedback path comes from the Q output of the leftmost FF.
- Find the primitive polynomial of the form $x^k + \dots + 1$.
- The $x^0 = 1$ term corresponds to connecting the feedback directly to the D input of FF 1.
- Each term of the form x^n corresponds to connecting an xor between FF n and $n+1$.
- 4-bit example, uses $x^4 + x + 1$
 - $x^4 \Leftrightarrow$ FF4's Q output
 - $x \Leftrightarrow$ xor between FF1 and FF2
 - $1 \Leftrightarrow$ FF1's D input
- To build an 8-bit LFSR, use the primitive polynomial $x^8 + x^4 + x^3 + x^2 + 1$ and connect xors between FF2 and FF3, FF3 and FF4, and FF4 and FF5.

  



Generating Polynomials

- **CRC-16: $G(x) = x^{16} + x^{15} + x^2 + 1$**
 - detects single and double bit errors
 - All errors with an odd number of bits
 - Burst errors of length 16 or less
 - Most errors for longer bursts
- **CRC-32: $G(x) = x^{32} + x^{26} + x^{23} + x^{22} + x^{16} + x^{12} + x^{11} + x^{10} + x^8 + x^7 + x^5 + x^4 + x^2 + x + 1$**
 - Used in ethernet
 - Also 32 bits of 1 added on front of the message
 - » Initialize the LFSR to all 1s