

VERILOG

Hardware Description Language

About Verilog

- **Along with VHDL, Verilog is among the most widely used HDLs.**
- **Main differences:**
 - **VHDL was designed to support system-level design and specification.**
 - **Verilog was designed primarily for digital hardware designers developing FPGAs and ASICs.**

Concept of Verilog “Module”

- In Verilog, the basic unit of hardware is called a module.
 - Modules cannot contain definitions of other modules.
 - A module can, however, be instantiated within another module.
 - Allows the creation of a *hierarchy* in a Verilog description.

Basic Syntax of Module Definition

```
module module_name (list_of_ports);  
  
    input/output declarations;  
  
    local net declarations;  
  
    parallel statements;  
  
endmodule
```

Example 1 :: simple AND gate

```
module simpleand (f, x, y);  
  input x, y;  
  output f;  
  assign f = x & y;  
endmodule
```

Example 2 :: two-level circuit

```
module two_level (a, b, c, d, f);  
  input a, b, c, d;  
  output f;  
  wire t1, t2;  
  assign t1 = a & b;  
  assign t2 = ~ (c | d);  
  assign f = t1 ^ t2;  
endmodule
```

Variable Data Types

- A variable belongs to one of two data types:
 - Net
 - Must be continuously driven
 - Used to model connections between continuous assignments & instantiations
 - Register
 - Retains the last value assigned to it
 - Often used to represent storage elements

CAD for VLSI

7

Net data type

- Different 'net' types supported for synthesis:
 - *wire, wor, wand, tri, supply0, supply1*
- 'wire' and 'tri' are equivalent; when there are multiple drivers driving them, the outputs of the drivers are shorted together.
- 'wor' / 'wand' inserts an OR / AND gate at the connection.
- 'supply0' / 'supply1' model power supply connections.

CAD for VLSI

8

```
module using_wired_and (A, B, C, D, f);  
  input  A, B, C, D;  
  output f;  
  wand  f;      // net f declared as 'wand'  
  
  assign f = A & B;  
  assign f = C | D;  
endmodule
```

```
module using_supply_wire (A, B, C, f);  
  input  A, B, C;  
  output f;  
  supply0 gnd;  
  supply1 vdd;  
  nand  G1 (t1, vdd, A, B);  
  xor   G2 (t2, C, gnd);  
  and   G3 (f, t1, t2);  
endmodule
```

Register data type

- Different ‘register’ types supported for synthesis:
 - **reg, integer**
- The ‘reg’ declaration explicitly specifies the size.
 - reg x, y; // single-bit register variables**
 - reg [15:0] bus; // 16-bit bus, bus[15] MSB**
- For ‘integer’, it takes the default size, usually 32-bits.
 - **Synthesizer tries to determine the size.**

Other differences:

- In arithmetic expressions,
 - An ‘integer’ is treated as a 2’s complement signed integer.
 - A ‘reg’ is treated as an unsigned quantity.
- General rule of thumb
 - ‘reg’ used to model actual hardware registers such as counters, accumulator, etc.
 - ‘integer’ used for situations like loop counting.

```

module simple_counter (clk, rst, count);
  input  clk, rst;
  output count;
  reg [31:0] count;

  always @(posedge clk)
  begin
    if (rst)
      count = 32'b0;
    else
      count = count + 1;
  end
endmodule

```

- When 'integer' is used, the synthesis system often carries out a data flow analysis of the model to determine its actual size.

- Example:

```

wire [1:10] A, B;
integer    C;
C = A + B;

```

- The size of C can be determined to be equal to 11 (ten bits plus a carry).

Specifying Constant Values

- A value may be specified in either the 'sized' or the 'un-sized' form.
 - Syntax for 'sized' form:
`<size>'<base><number>`
- Examples:
 - `8'b01110011 // 8-bit binary number`
 - `12'hA2D // 1010 0010 1101 in binary`
 - `12'hCx5 // 1100 xxxx 0101 in binary`
 - `25 // signed number, 32 bits`
 - `1'b0 // logic 0`
 - `1'b1 // logic 1`

CAD for VLSI

15

Parameters

- A *parameter* is a constant with a name.
- No size is allowed to be specified for a parameter.
 - The size gets decided from the constant itself (32-bits if nothing is specified).
- Examples:
 - `parameter HI = 25, LO = 5;`
 - `parameter up = 2b'00, down = 2b'01,`
`steady = 2b'10;`

CAD for VLSI

16

Logic Values

- The common values used in modeling hardware are:
 - 0 :: Logic-0 or FALSE
 - 1 :: Logic-1 or TRUE
 - x :: Unknown (or don't care)
 - z :: High impedance
- Initialization:
 - All unconnected nets set to 'z'
 - All register variables set to 'x'

- Verilog provides a set of predefined logic gates.
 - They respond to inputs (0, 1, x, or z) in a logical way.
 - Example :: AND
 - 0 & 0 → 0
 - 0 & 1 → 0
 - 1 & 1 → 1
 - 1 & x → x
 - 0 & x → 0
 - 1 & z → x
 - z & x → x

Primitive Gates

- **Primitive logic gates (instantiations):**

```
and  G (out, in1, in2);
nand G (out, in1, in2);
or   G (out, in1, in2);
nor  G (out, in1, in2);
xor  G (out, in1, in2);
xnor G (out, in1, in2);
not  G (out1, in);
buf  G (out1, in);
```

- **Primitive Tri-State gates (instantiation)**

```
bufif1 G (out, in, ctrl);
bufif0 G (out, in, ctrl);
notif1 G (out, in, ctrl);
notif0 G (out, in, ctrl);
```

Some Points to Note

- For all primitive gates,
 - The output port must be connected to a net (a wire).
 - The input ports may be connected to nets or register type variables.
 - They can have a single output but any number of inputs.
 - An optional delay may be specified.
 - *Logic synthesis tools ignore time delays.*

```
`timescale 1 ns / 1ns
module exclusive_or (f, a, b);
    input a, b;
    output f;
    wire t1, t2, t3;
    nand #5 m1 (t1, a, b);
    and #5 m2 (t2, a, t1);
    and #5 m3 (t3, t1, b);
    or #5 m4 (f, t2, t3);
endmodule
```

Hardware Modeling Issues

- The values computed can be held in
 - A 'wire'
 - A 'flip-flop' (edge-triggered storage cell)
 - A 'latch' (level-sensitive storage cell)
- A variable in Verilog can be of
 - 'net data type'
 - Maps to a 'wire' during synthesis
 - 'register' data type
 - Maps either to a 'wire' or to a 'storage cell' depending on the context under which a value is assigned.

CAD for VLSI

23

```
module reg_maps_to_wire (A, B, C, f1, f2);
  input  A, B, C;
  output f1, f2;
  wire  A, B, C;
  reg   f1, f2;
  always @(A or B or C)
  begin
    f1 = ~(A & B);
    f2 = f1 ^ C;
  end
endmodule
```

The synthesis system
will generate a wire
for f1

CAD for VLSI

24

```

module a_problem_case (A, B, C, f1, f2);
  input  A, B, C;
  output f1, f2;
  wire  A, B, C;
  reg   f1, f2;
  always @(A or B or C)
  begin
    f2 = f1 ^ f2;
    f1 = ~(A & B);
  end
endmodule

```

The synthesis system will not generate a storage cell for f1

CAD for VLSI

25

```

// A latch gets inferred here
module simple_latch (data, load, d_out);
  input  data, load;
  output d_out;

  always @(load or data)
  begin
    if (!load)
      t = data;
      d_out = !t;
  end
endmodule

```

Else part missing; so latch is inferred.

CAD for VLSI

26

Verilog Operators

- Arithmetic operators

`*`, `/`, `+`, `-`, `%`

- Logical operators

`!` → logical negation

`&&` → logical AND

`||` → logical OR

- Relational operators

`>`, `<`, `>=`, `<=`, `==`, `!=`

- Bitwise operators

`~`, `&`, `|`, `^`, `~^`

CAD for VLSI

27

- Reduction operators (operate on all the bits within a word)

`&`, `~&`, `|`, `~|`, `^`, `~^`

→ accepts a single word operand and produces a single bit as output

- Shift operators

`>>`, `<<`

- Concatenation `{ }`

- Replication `{ n { } }`

- Conditional

`<condition> ? <expression1> : <expression2>`

CAD for VLSI

28

```
// An 8-bit adder description
```

```
module parallel_adder (sum, cout, in1, in2, cin);  
  input  [7:0] in1, in2;  input  cin;  
  output [7:0] sum;      output cout;  
  
  assign #20 {cout, sum} = in1 + in2 + cin;  
endmodule
```

Some Points

- The presence of a 'z' or 'x' in a *reg* or *wire* being used in an arithmetic expression results in the whole expression being unknown ('x').
- The logical operators (!, &&, | |) all evaluate to a 1-bit result (0, 1 or x).
- The relational operators (>, <, <=, >=, ~=, ==) also evaluate to a 1-bit result (0 or 1).
- Boolean *false* is equivalent to 1'b0
Boolean *true* is equivalent to 1'b1.

Some Valid Statements

```
assign outp = (p == 4'b1111);  
if (load && (select == 2'b01)) .....  
assign a = b >> 1;  
assign a = b << 3;  
assign f = {a, b};  
assign f = {a, 3'b101, b};  
assign f = {x[2], y[0], a};  
assign f = { 4{a} }; // replicate four times  
assign f = {2'b10, 3{2'b01}, x};
```

Description Styles in Verilog

- **Two different styles of description:**
 1. **Data flow**
 - **Continuous assignment**
 2. **Behavioral**
 - **Procedural assignment**
 - ❖ **Blocking**
 - ❖ **Non-blocking**

Data-flow Style: Continuous Assignment

- Identified by the keyword “assign”.
 assign a = b & c;
 assign f[2] = c[0];
- Forms a static binding between
 - The ‘net’ being assigned on the LHS,
 - The expression on the RHS.
- The assignment is continuously active.
- Almost exclusively used to model combinational logic.

- A Verilog module can contain any number of continuous assignment statements.
- For an “assign” statement,
 - The expression on RHS may contain both “register” or “net” type variables.
 - The LHS must be of “net” type, typically a “wire”.
- Several examples of “assign” illustrated already.

```
module generate_mux (data, select, out);  
  input [0:7] data;  
  input [0:2] select;  
  output out;  
  
  assign out = data [select];  
endmodule
```

**Non-constant index in
expression on RHS
generates a MUX**

CAD for VLSI

35

```
module generate_decoder (out, in, select);  
  input in;  
  input [0:1] select;  
  output [0:3] out;  
  
  assign out [select] = in;  
endmodule
```

**Non-constant index in
expression on LHS
generates a decoder**

CAD for VLSI

36

```
module generate_set_of_MUX (a, b, f, sel);  
  input [0:3] a, b;  
  input sel;  
  output [0:3] f;  
  
  assign f = sel ? a : b;  
endmodule
```

Conditional operator
generates a MUX

```
module level_sensitive_latch (D, Q, En);  
  input D, En;  
  output Q;  
  
  assign Q = en ? D : Q;  
endmodule
```

Using “assign” to describe
sequential logic

Behavioral Style: Procedural Assignment


- The procedural block defines
 - A region of code containing *sequential* statements.
 - The statements execute in the order they are written.
- Two types of procedural blocks in Verilog
 - The “always” block
 - A continuous loop that never terminates.
 - The “initial” block
 - Executed once at the beginning of simulation (used in Test-benches).

CAD for VLSI

39

- A module can contain any number of “always” blocks, all of which execute concurrently.
- Basic syntax of “always” block:
 
```
always @(event_expression)
begin
    statement;
    statement;
end
```



Sequential statements

- The @(event_expression) is required for both combinational and sequential logic descriptions.

CAD for VLSI

40

- Only “reg” type variables can be assigned within an “always” block.

Sequential Statements in Verilog

1. **begin**
 sequential_statements
 end
2. **if (expression)**
 sequential_statement
 [else
 sequential_statement]
3. **case (expression)**
 expr: sequential_statement

 default: sequential_statement
 endcase

**begin...end
not required
if there
is only 1 stmt.**

4. **forever**
 sequential_statement
5. **repeat (expression)**
 sequential_statement
6. **while (expression)**
 sequential_statement
7. **for (expr1; expr2; expr3)**
 sequential_statement

8. **# (time_value)**
 - **Makes a block suspend for “time_value” time units.**
9. **@ (event_expression)**
 - **Makes a block suspend until event_expression triggers.**

```
// A combinational logic example
```

```
module mux21 (in1, in0, s, f);  
  input in1, in0, s;  
  output f;  
  reg f;  
  
  always @ (in1 or in0 or s)  
    if (s)  
      f = in1;  
    else  
      f = in0;  
endmodule
```

CAD for VLSI

45

```
// A sequential logic example
```

```
module dff_negedge (D, clock, Q, Qbar);  
  input D, clock;  
  output Q, Qbar;  
  reg Q, Qbar;  
  
  always @ (negedge clock)  
    begin  
      Q = D;  
      Qbar = ~D;  
    end  
endmodule
```

CAD for VLSI

46

// Another sequential logic example

```
module incomp_state_spec (curr_state, flag);  
  input  [0:1] curr_state;  
  output [0:1] flag;  
  reg    [0:1] flag;  
  
  always @ (curr_state)  
    case (curr_state)  
      0, 1 : flag = 2;  
      3    : flag = 0;  
    endcase  
endmodule
```

The variable 'flag' is not assigned a value in all the branches of case.
→ Latch is *inferred*

CAD for VLSI

47

// A small change made

```
module incomp_state_spec (curr_state, flag);  
  input  [0:1] curr_state;  
  output [0:1] flag;  
  reg    [0:1] flag;  
  
  always @ (curr_state)  
    flag = 0;  
    case (curr_state)  
      0, 1 : flag = 2;  
      3    : flag = 0;  
    endcase  
endmodule
```

'flag' defined for all values of curr_state.
→ Latch is *avoided*

CAD for VLSI

48

```

module ALU_4bit (f, a, b, op);
  input [1:0] op;    input [3:0] a, b;
  output [3:0] f;    reg [3:0] f;

  parameter ADD=2'b00, SUB=2'b01,
            MUL=2'b10, DIV=2'b11;

  always @ (a or b or op)
    case (op)
      ADD : f = a + b;
      SUB : f = a - b;
      MUL : f = a * b;
      DIV : f = a / b;
    endcase
endmodule

```

CAD for VLSI

49

Blocking & Non-blocking Assignments

- Sequential statements within procedural blocks (“always” and “initial”) can use two types of assignments:
 - Blocking assignment
 - Uses the ‘=’ operator
 - Non-blocking assignment
 - Uses the ‘<=’ operator

CAD for VLSI

50

Blocking Assignment (using '=')

- Most commonly used type.
- The target of assignment gets updated before the next sequential statement in the procedural block is executed.
- A statement using blocking assignment blocks the execution of the statements following it, until it gets completed.
- Recommended style for modeling combinational logic.

Non-Blocking Assignment (using '<=')

- The assignment to the target gets scheduled for the end of the simulation cycle.
 - Normally occurs at the end of the sequential block.
 - Statements subsequent to the instruction under consideration are not blocked by the assignment.
- Recommended style for modeling sequential logic.
 - Can be used to assign several 'reg' type variables synchronously, under the control of a common clock.

Some Rules to be Followed

- Verilog synthesizer ignores the delays specified in a procedural assignment statement.
- A variable cannot appear as the target of *both* a blocking and a non-blocking assignment.
 - Following is not permissible:

```
value = value + 1;  
value <= init;
```

CAD for VLSI

53

// Up-down counter (synchronous clear)

```
module counter (mode, clr, ld, d_in, clk, count);  
input mode, clr, ld, clk;   input [0:7] d_in;  
output [0:7] count;        reg [0:7] count;  
always @ (posedge clk)  
    if (ld)  
        count <= d_in;  
    else if (clr)  
        count <= 0;  
    else if (mode)  
        count <= count + 1;  
    else  
        count <= count - 1;  
endmodule
```

CAD for VLSI

54

```
// Parameterized design:: an N-bit counter
```

```
module counter (clear, clock, count);
```

```
parameter N = 7;
```

```
input clear, clock;
```

```
output [0:N] count;      reg [0:N] count;
```

```
always @ (negedge clock)
```

```
  if (clear)
```

```
    count <= 0;
```

```
  else
```

```
    count <= count + 1;
```

```
endmodule
```

CAD for VLSI

55

```
// Using more than one clocks in a module
```

```
module multiple_clk (clk1, clk2, a, b, c, f1, f2);
```

```
input clk1, clk2, a, b, c;
```

```
output f1, f2;
```

```
reg f1, f2;
```

```
always @ (posedge clk1)
```

```
  f1 <= a & b;
```

```
always @ (negedge clk2)
```

```
  f2 <= b ^ c;
```

```
endmodule
```

CAD for VLSI

56

```

// Using multiple edges of the same clock

module multi_phase_clk (a, b, f, clk);
  input a, b, clk;
  output f;
  reg f, t;
  always @ (posedge clk)
    f <= t & b;
  always @ (negedge clk)
    t <= a | b;
endmodule

```

CAD for VLSI

57

A Ring Counter Example

```

module ring_counter (clk, init, count);
  input clk, init;   output [7:0] count;
  reg [7:0] count;
  always @ (posedge clk)
  begin
    if (init)
      count = 8'b10000000;
    else begin
      count  = count << 1;
      count[0] = count[7];
    end
  end
endmodule

```



CAD for VLSI

58

A Ring Counter Example (Modified)

```
module ring_counter_modi1 (clk, init, count);
input clk, init;    output [7:0] count;
reg [7:0] count;
always @ (posedge clk)
begin
    if (init)
        count = 8'b10000000;
    else begin
        count    <= count << 1;
        count[0] <= count[7];
    end
end
endmodule
```

CAD for VLSI

59

About “Loop” Statements

- Verilog supports four types of loops:
 - ‘while’ loop
 - ‘for’ loop
 - ‘forever’ loop
 - ‘repeat’ loop
- Many Verilog synthesizers supports only ‘for’ loop for synthesis:
 - Loop bound must evaluate to a constant.
 - Implemented by unrolling the ‘for’ loop, and replicating the statements.

CAD for VLSI

60

Modeling Memory

- Synthesis tools are usually not very efficient in synthesizing memory.
 - Best modeled as a component.
 - Instantiated in a design.
- Implementing memory as a two-dimensional register file is inefficient.

```
module memory_example (en, clk, adbus, dbus,  
                      rw);  
  
    parameter N = 16;  
    input en, rw, clk;  
    input [N-1:0] adbus;  
    output [N-1:0] dbus;  
  
    .....  
    ROM Mem1 (clk, en, rw, adbus, dbus);  
  
    .....  
endmodule
```

Modeling Tri-state Gates

```
module bus_driver (in, out, enable);  
  input enable;      input [0:7] in;  
  output [0:7] out;  reg [0:7] out;  
  
  always @ (enable or in)  
    if (enable)  
      out = in;  
    else  
      out = 8'bz;  
endmodule;
```


CAD for VLSI

63


Modeling Finite State Machines

- Two types of FSMs

- Moore Machine

 

- Mealy Machine

 


CAD for VLSI

64

Moore Machine : Example 1

- **Traffic Light Controller**

 - Simplifying assumptions made
- Three lights only (RED, GREEN, YELLOW)
- The lights glow cyclically at a fixed rate
 - Say, 10 seconds each
 - The circuit will be driven by a clock of appropriate frequency



CAD for VLSI

65

```
module traffic_light (clk, light);
  input clk;
  output [0:2] light;  reg [0:2] light;
  parameter S0=0, S1=1, S2=2;
  parameter RED=3'b100, GREEN=3'b010,
            YELLOW=3'b001;
  reg [0:1] state;
  always @ (posedge clk)
    case (state)
      S0: begin          // S0 means RED
            light <= YELLOW;
            state <= S1;
          end
    end
```

CAD for VLSI

66

```

S1: begin                // S1 means YELLOW
    light <= GREEN;
    state <= S2;
end
S2: begin                // S2 means GREEN
    light <= RED;
    state <= S0;
end
default: begin
    light <= RED;
    state <= S0;
end
endcase
endmodule

```

CAD for VLSI

67

- **Comment on the solution**
 - **Five flip-flops are synthesized**
 - **Two for 'state'**
 - **Three for 'light' (outputs are also latched into flip-flops)**
 - **If we want non-latched outputs, we have to modify the Verilog code.**
 - **Assignment to 'light' made in a separate 'always' block.**
 - **Use blocking assignment.**

CAD for VLSI

68

```

module traffic_light_nonlatched_op (clk, light);
  input clk;
  output [0:2] light;   reg [0:2] light;
  parameter S0=0, S1=1, S2=2;
  parameter RED=3'b100, GREEN=3'b010,
             YELLOW=3'b001;

  reg [0:1] state;
  always @ (posedge clk)
    case (state)
      S0:    state <= S1;
      S1:    state <= S2;
      S2:    state <= S0;
      default: state <= S0;
    endcase

```

CAD for VLSI

69

```

  always @ (state)
    case (state)
      S0:    light = RED;
      S1:    light = YELLOW;
      S2:    light = GREEN;
      default: light = RED;
    endcase
  endmodule


```

CAD for VLSI

70

Moore Machine: Example 2

- Serial parity detector

 

CAD for VLSI

71

```
module parity_gen (x, clk, z);
  input x, clk;
  output z;    reg z;
  reg even_odd; // The machine state
  parameter EVEN=0, ODD=1;

  always @(posedge clk)
    case (even_odd)
      EVEN: begin
        z <= x ? 1 : 0;
        even_odd <= x ? ODD : EVEN;
      end
    end
end
```

CAD for VLSI

72

```


ODD: begin
    z <= x ? 0 : 1;
    even_odd <= x ? EVEN : ODD;
end
endcase
endmodule

```

- If no output latches need to be synthesized, we can follow the principle shown in the last example.

 Example with Multiple Modules

- A simple example showing multiple module definitions.



```

module complementor (Y, X, comp);
  input [7:0] X;
  input comp;
  output [7:0] Y;   reg [7:0] Y;

  always @ (X or comp)
    if (comp)
      Y = ~X;
    else
      Y = X;
endmodule

```

```

module adder (sum, cy_out, in1, in2, cy_in);
  input [7:0] in1, in2;
  input cy_in;
  output [7:0] sum;   reg [7:0] sum;
  output cy_out;     reg cy_out;

  always @ (in1 or in2 or cy_in)
    {cy_out, sum} = in1 + in2 + cy_in;
endmodule

```

```

module parity_checker (out_par, in_word);
  input [8:0] in_word;
  output out_par;

  always @ (in_word)
    out_par = ^ (in_word);
endmodule

```

```

// Top level module
module add_sub_parity (p, a, b, add_sub);
  input [7:0] a, b;
  input add_sub; // 0 for add, 1 for subtract
  output p; // parity of the result
  wire [7:0] Bout, sum; wire carry;

  complementor M1 (Bout, B, add_sub);
  adder M2 (sum, carry, A, Bout, add_sub);
  parity_checker M3 (p, {carry, sum});
endmodule


```

Verilog Test Bench



Introduction

 - **What is test bench?**
 - A Verilog procedural block which executes only once.
 - Used for simulation.
 - Testbench generates clock, reset, and the required test vectors.



How to Write Testbench?

- **Create a dummy template**
 - Declare inputs to the module-under-test (MUT) as “reg”, and the outputs as “wire”.
 - Instantiate the MUT.
- **Initialization**
 - Assign some known values to the MUT inputs.
- **Clock generation logic**
 - Various ways to do so.
- **May include several simulator directives**
 - Like \$display, \$monitor, \$dumpfile, \$dumpvars, \$finish.

- **\$display**
 - Prints text or variables to stdout.
 - Syntax same as “printf”.
- **\$monitor**
 - Similar to \$display, but prints the value whenever the value of some variable in the given list changes.
- **\$finish**
 - Terminates the simulation process.
- **\$dumpfile**
 - Specify the file that will be used for storing the waveform.
- **\$dumpvars**
 - Starts dumping all the signals to the specified file.

Example Test Bench

```

module shifter_toplevel;
  reg clk, clear, shift;
  wire [7:0] data;

  shift_register S1 (clk, clear, shift, data);
  initial
  begin
    clk = 0; clear = 0; shift = 0;
  end
  always
  #10 clk = !clk;
endmodule

```

Test Bench: More Complete Version

```
module shifter_toplevel;
  reg clk, clear, shift;
  wire [7:0] data;

  shift_register S1 (clk, clear, shift, data);
  initial
  begin
    clk = 0; clear = 0; shift = 0;
  end
  always
    #10 clk = !clk;

```

contd..

CAD for VLSI

85

```
  initial
  begin
    $dumpfile ("shifter.vcd");
    $dumpvars;
  end
  initial
  begin
    $display ("\ttime, \tclk, \tclr, \tsft, \tdata");
    $monitor ("%d, %d, %d, %d, %d", $time,
              clk, reset, clear, shift, data);
  end
  initial
    #400 $finish;
  ***** REMAINING CODE HERE *****
endmodule
```

CAD for VLSI

86

A Complete Example

```
module testbench;  
  wire w1, w2, w3;  
  xyz m1 (w1, w2, w3);  
  test_xyz m2 (w1, w2, w3);  
endmodule
```

```
module xyz (f, A, B);  
  input A, B;  output f;  
  nor #1 (f, A, B);  
endmodule
```

contd..

CAD for VLSI

87

```
module test_xyz (f, A, B);  
  input f;  
  output A, B;  
  reg A, B;  
  initial  
  begin  
    $monitor ($time, "A=%b", "B=%b", f=%b",  
              A, B, f);  
  
    #10 A = 0; B = 0;  
    #10 A = 1; B = 0;  
    #10 A = 1; B = 1;  
    #10 $finish;  
  end  
endmodule
```

CAD for VLSI

88

Pipelining Example

- Consider the following arithmetic computation:

$$X = (A + B) * (B - C + D)$$

$$Y = (B - C + D)$$

- Suppose we break into three stages:

- **S1:** $S1_T1 = A+B$; $S1_T2 = B-C$; $S1_T3 = D$;

- **S2:** $S2_T1 = S1_T1$; $S2_T4 = S1_T2 + S1_T3$;

- **S3:** $S3_X = S2_T1 * S2_T4$; $S3_Y = S2_T4$;

```
module pipeline_example (A, B, C, D, X, Y, clk);
  input [0:7] A, B, C, D, clk;
  output X, Y;
  wire [0:18] X; wire [0:9] Y;
  reg [0:8] S1_T1, S2_T1, S1_T2;
  reg [0:7] S1_T3; reg [0:9] S2_T4, S3_Y; reg [0:18] S3_X;

  assign X = S3_X; assign Y = S3_Y;
  always @(posedge clk)
  begin
    S1_T1 <= A + B; S1_T2 <= B - C; S1_T3 <= D;
    S2_T1 <= S1_T1; S2_T4 <= S1_T2 + S1_T3;
    S3_X <= S2_T1 * S2_T4; S3_Y <= S2_T4;
  end;
endmodule
```