

Decoders

- A **full decoder** with n inputs has 2^n outputs. Let inputs be labeled $In_0, In_1, In_2, \dots, In_{n-1}$, and let outputs be labeled $Out_0, Out_1, \dots, Out_{2^n-1}$.
- A full decoder functions as follows: Only one of outputs has value 1 (it is active) while all other outputs have value 0. The only output set to 1 is one labeled with the decimal value equal to the (binary) value on input lines.
- In general, a decoder with n inputs may have fewer than 2^n outputs. Sometime those are called **partial decoders**.

3-Input Full Decoder

 


Figure B.3.1

Multiplexers

- A **basic multiplexer** has only one output line z . There are two sets of input lines: data lines and select lines.
- Let a number of data lines be N , labeled $d_0, d_1, d_2, \dots, d_{N-1}$. There are m select lines, labeled s_0, s_1, \dots, s_{m-1} . m is such that any of data lines can be referenced (selected) by a decimal value on select lines. Thus, m has to satisfy the following inequality: $2^{m-1} < N \leq 2^m$.
- A multiplexer functions as follows: Output z has the value of the data input line labeled by a decimal value equal to a (binary) value on select lines.

Simplest Basic Multiplexer

Simplest mux is one with 2 data input lines and 1 select line.

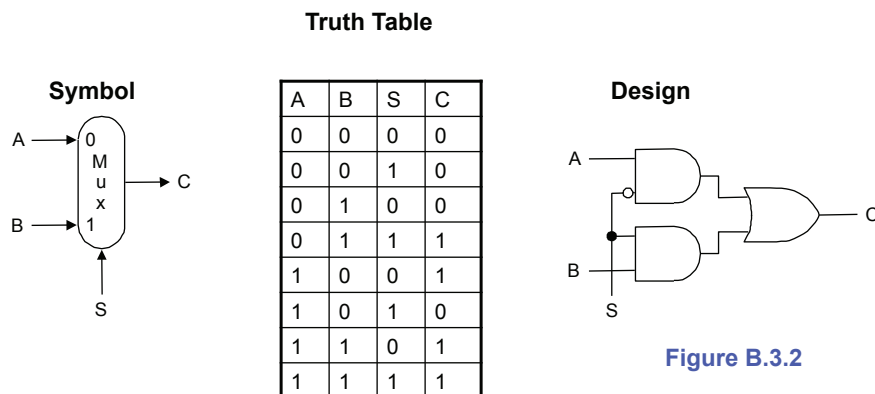


Figure B.3.2

3-Data Multiplexer Truth Table

d0	d1	d2	s1	s0	z
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	d
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	1
0	0	1	1	1	d
0	1	0	0	0	0
0	1	0	0	1	1
0	1	0	1	0	0
0	1	0	1	1	d
0	1	1	0	0	0
-	-	-	-	-	-
1	1	1	1	0	1
1	1	1	1	1	d

This input not allowed

This input not allowed

This input not allowed


g. babic

Presentation D

21

Complex Multiplexer

 - Instead N single data lines and one output line as in a basic mux, a complex mux has N sets of data lines and one set of output lines and each set has K lines.
- No changes with select lines.



N=2, K=32

Design of mux on left at basic mux level

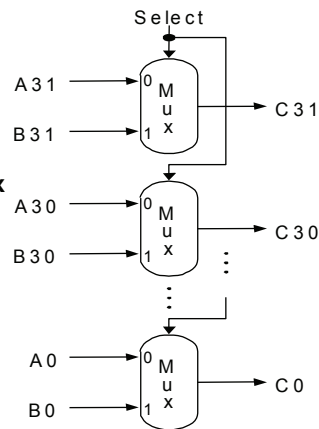


Figure B.3.6


g. babic

Presentation D

22

R-S Latch: Simplest Sequential Circuit

A	B	A nor B
0	0	1
0	1	0
1	0	0
1	1	0

 

1. Let us start with: $S = 0$ & $R = 1 \rightarrow Qa = 0$ & $Qb = 1$
2. Let us now change R to 0: $S = 0$ & $R = 0 \rightarrow Qa = 0$ & $Qb = 1 \rightarrow$ no change
3. Let us now change S to 1: $S = 1$ & $R = 0 \rightarrow Qa = 1$ & $Qb = 0$
4. Let us now change S to 0: $S = 0$ & $R = 0 \rightarrow Qa = 1$ & $Qb = 0 \rightarrow$ no change

Thus, for steps 2 and 4 inputs are identical while outputs are different, i.e. we have a sequential circuit.

Study: B.7 & B.8

g. babic


Presentation D

23

R-S Latch Characteristics

R-S latch is a memory element that “remembers” which of two inputs has most recently had value 1:

 - Outputs $Qa = 1$ & $Qb = 0$ indicate that S is currently or was 1 last
- Outputs $Qa = 0$ & $Qb = 1$ indicate that R is currently or was 1 last




g. babic

Presentation D

24

R-S Latch Characteristics (continued)

A	B	A nor B
0	0	1
0	1	0
1	0	0
1	1	0

 

5. Let us consider case: $S = 1$ & $R = 1 \rightarrow Qa = 0$ & $Qb = 0$

$Qa = 0$ & $Qb = 0$ indicate that currently $S = 1$ and $R = 1$

6a. Let us now change S to 0: $S = 0$ & $R = 1 \rightarrow Qa = 0$ & $Qb = 1$,

\rightarrow Identical to Step 1 on Slide 21


g. babic

Presentation D

25

R-S Latch Characteristics (continued)

A	B	A nor B
0	0	1
0	1	0
1	0	0
1	1	0

 

5. Let us again consider case: $S = 1$ & $R = 1 \rightarrow Qa = 0$ & $Qb = 0$

6b. Let us now change S and R simultaneously to 0: $S = 0$ & $R = 0$

\rightarrow Unstable state


Note: Set=Reset=1 at the same time should be avoided

g. babic

Presentation D

26

Gated (Clocked) R-S Latch

 


- C input is write enable
- When $C = 1$, a gated R-S latch behaves as an ordinary R-S latch, since $R'=R$ and $S'=S$.
- When $C = 0$, changes in R and S do not influence outputs.
- Note that the case $R'=1$ & $S'=1$ is still possible, and then an unstable state can be reached easily. How?

g. babic

Presentation D

27

(Gated) D-Latch

 


- Two inputs:
 - the data value to be stored (D)
 - the write enable signal (C) indicating when to read & store D
- Two outputs:
 - the value of the internal state (Q) and its complement (often unused)
- Note: The case $R'=1$ & $S'=1$ is not possible.

g. babic

Presentation D

28

D-Latch Functioning

 


- *D-latch functions as follows:*
 - when $C=1$, D-latch state (and Q-output) is identical to D-input, i.e. any change in the value of D-input is 'immediately' followed by the change of Q-output.
 - When $C=0$, D-latch state is unchanged and it keeps the value it had at the time when C input changed from 1 to 0.

g. babic

Presentation D

29

D Flip-Flop

 


- Two inputs:
 - the data value to be stored (D)
 - the write enable signal (C) indicating when to read & store D
- Two outputs:
 - the value of the internal state (Q) and it's complement (often unused)

g. babic

Presentation D

30

D Flip-Flop Functioning

 

- *D-flip-flop functions as follows:*
 - When C changes its value from 1 to 0, i.e. on the falling edge, D-flip flop state (and Q output) gets the value D-input has at that moment,
 - During all other times, D-flip flop state is unchanged and it keeps the value it had at the time of the falling edge of C-input.

Presentation D

31

Set-up and Hold Time

- There is critical period T_{cr} around the falling edge of C during which value on D should not change. T_{cr} is split into two parts, the setup time before the C edge, and the hold time after the C edge.
- **The setup time** is the minimum time the D signal must be stable before the C signal falling edge .
- **The hold time** is the minimum time the D signal must be stable after C signal falling edge.



Figure B.8.6

- Failure to meet these minimum requirements can result in a situation where the output of the flip-flop may not be predictable.
- Note that hold times are usually either 0 or very small and thus not a major concern.

g. babic

Presentation D

32

Register File Design

- Register file = set of registers that can be read/written by supplying a register number
- D flip-flop - building block

- Typical register file has:


- 2 read ports
- 1 write port

- **Read operation:**

- supply reg# at input
- output on Read data line

- **Write operation:**

- select reg#
- set write data signal

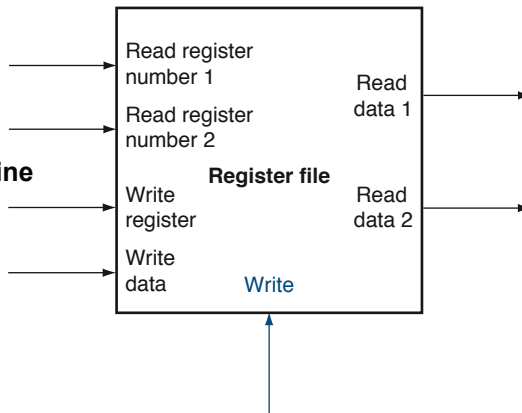

g. babic

33