 





ECE468 Computer Organization & Architecture ALU Design II

Review: A One Bit ALU

- This 1-bit ALU will perform AND, OR, and ADD



 Review: Functional Specification of the ALU



ALU Control Lines (ALUOp)

- 000
- 001
- 010
- 110
- 111

Function
And
Or
Add
Subtract
Set-on-less-than

Deriving requirements of ALU

- Start with instruction set architecture: must be able to do all operations in ISA
- Tradeoffs of cost and speed based on frequency of occurrence, hardware budget
- MIPS ISA

MIPS arithmetic instructions

Instruction	Example	Meaning	Comments
add	add \$1,\$2,\$3	$S1 = S2 + S3$	3 operands; exception possible
subtract	sub \$1,\$2,\$3	$S1 = S2 - S3$	3 operands; exception possible
add immediate	addi \$1,\$2,100	$S1 = S2 + 100$	+ constant; exception possible
add unsigned	addu \$1,\$2,\$3	$S1 = S2 + S3$	3 operands; no exceptions
subtract unsigned	subu \$1,\$2,\$3	$S1 = S2 - S3$	3 operands; no exceptions
add imm. unsign.	addiu \$1,\$2,100	$S1 = S2 + 100$	+ constant; no exceptions
multiply	mult \$2,\$3	Hi, Lo = $S2 \times S3$	64-bit signed product
multiply unsigned	multu \$2,\$3	Hi, Lo = $S2 \times S3$	64-bit unsigned product
divide	div \$2,\$3	Lo = $S2 \div S3$, Hi = $S2 \text{ mod } S3$	Lo = quotient, Hi = remainder
divide unsigned	divu \$2,\$3	Lo = $S2 \div S3$, Hi = $S2 \text{ mod } S3$	Unsigned quotient & remainder
Move from Hi	mfi \$1	$S1 = Hi$	Used to get copy of Hi
Move from Lo	mflo \$1	$S1 = Lo$	Used to get copy of Lo

MIPS logical instructions

Instruction	Example	Meaning	Comment
and	and \$1,\$2,\$3	$S1 = S2 \& S3$	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	$S1 = S2 S3$	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	$S1 = S2 \oplus S3$	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	$S1 = \sim(S2 S3)$	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	$S1 = S2 \& 10$	Logical AND reg, constant
or immediate	ori \$1,\$2,10	$S1 = S2 10$	Logical OR reg, constant
xor immediate	xori \$1, \$2,10	$S1 = \sim S2 \oplus 10$	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	$S1 = S2 \ll 10$	Shift left by constant
shift right logical	srl \$1,\$2,10	$S1 = S2 \gg 10$	Shift right by constant
shift right arithm.	sra \$1,\$2,10	$S1 = S2 \gg 10$	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	$S1 = S2 \ll S3$	Shift left by variable
shift right logical	srlv \$1,\$2, \$3	$S1 = S2 \gg S3$	Shift right by variable
shift right arithm.	srav \$1,\$2, \$3	$S1 = S2 \gg S3$	Shift right arith. by variable

Compare and Branch

- Compare and Branch
 - BEQ rs, rt, offset if $R[rs] == R[rt]$ then PC-relative branch
 - BNE rs, rt, offset \lt
- Compare to zero and branch
 - BLEZ rs, offset if $R[rs] \leq 0$ then PC-relative branch
 - BGTZ rs, offset \gt
 - BLT \lt
 - BGEZ \geq
 - BLTZAL rs, offset if $R[rs] < 0$ then branch and link (into R 31)
 - BGEZAL \geq

MIPS ALU requirements


- Add, AddU, Sub, SubU, Addl, Addiu
 - \Rightarrow 2's complement adder with overflow detection & inverter
- SLTI, SLTIU (set less than)
 - \Rightarrow 2's complement adder with inverter, check sign bit of result
- BEQ, BNE (branch on equal or not equal)
 - \Rightarrow 2's complement adder with inverter, check if result = 0
- And, Or, Andl, Orl
 - \Rightarrow Logical AND, logical OR
- ALU from last lecture supports these ops

Additional MIPS ALU requirements

- Xor, Nor, Xorl
 - \Rightarrow Logical XOR, logical NOR or use 2 steps: (A OR B) XOR 1111....1111
- Sll, Srl, Sra
 - \Rightarrow Need left shift, right shift, right shift arithmetic by 0 to 31 bits
- Mult, MultU, Div, DivU
 - \Rightarrow Need 32-bit multiply and divide, signed and unsigned

Add XOR to ALU


- Expand Multiplexor

 


Shifters

Three different kinds:


logical-- value shifted in is always "0"

 

 arithmetic-- on right shifts, sign extend




 rotating-- shifted out bits are wrapped around (not in MIPS)




Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!

Multiplexor/Shifter

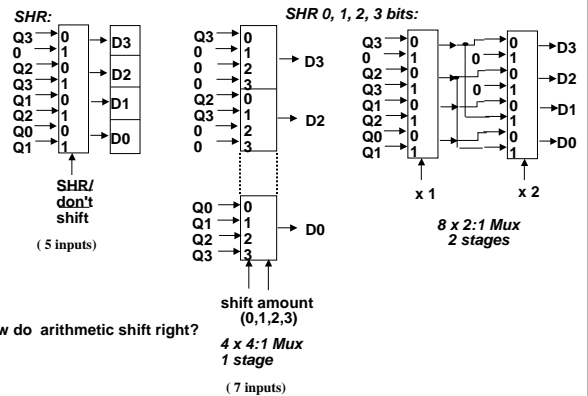

How do arithmetic shift right?

4 x 4:1 Mux
1 stage
(7 inputs)




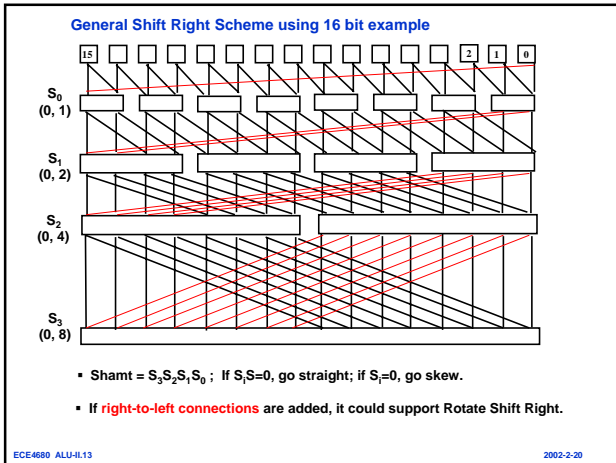


MULTIPLY (p250)

- ° Paper and pencil example:

Multiplicand		1000
Multiplier	x	1001
		1000
		0000
		0000
		1000
Product		1001000
- ° m bits x n bits = m+n bit product
- ° Binary makes it easy: only 2 choices at each step
 - 1 => place multiplicand (1 x multiplicand)
 - 0 => place 0 (0 x multiplicand)
- ° 3 versions of multiply hardware & algorithm: successive refinement


ECE4680 ALU-II.14 2002-2-20

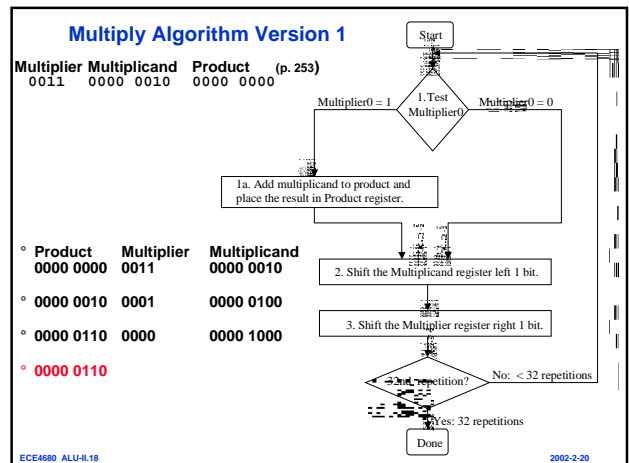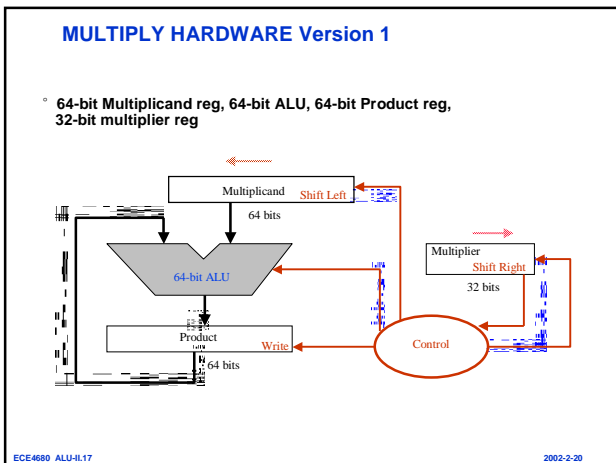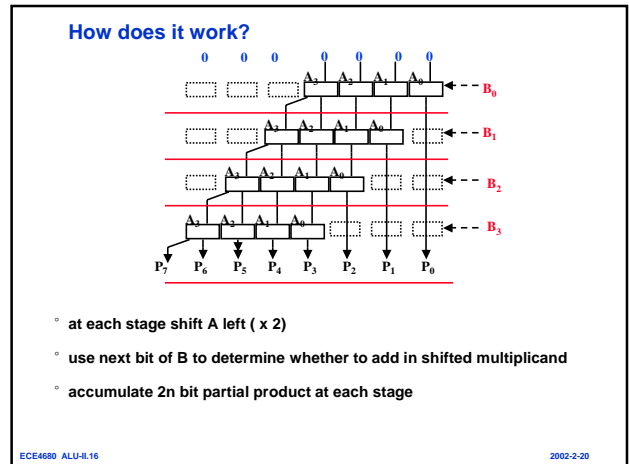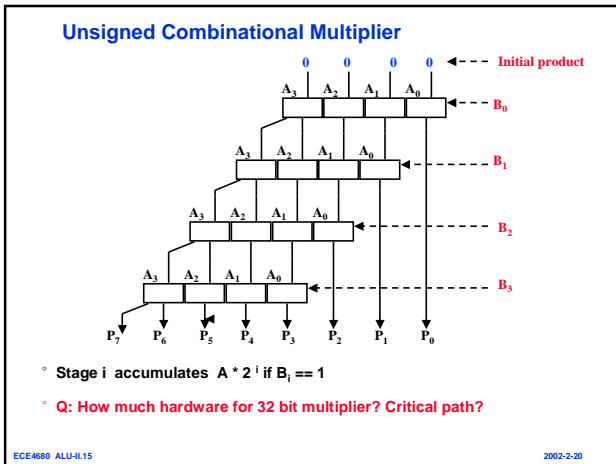

Observations on Multiply Version 1

- 1 clock cycle per step => ~ 100 cycles per multiply of two 32-bits.
 - Ratio of multiply to add 1:5 to 1:100.
 - Amdahl's Law: even a moderate frequency of a slow operation can limit performance.
- 1/2 bits in multiplicand always 0 => 64-bit adder is wasted
- 0 is inserted in left of multiplicand as shifted => least significant bits of product never changed once formed
- Very big, too slow.
- Instead of shifting multiplicand to left, shift product to right?


What's going on?

 

Multiplicand stays still and product moves right


MULTIPLY HARDWARE Version 2

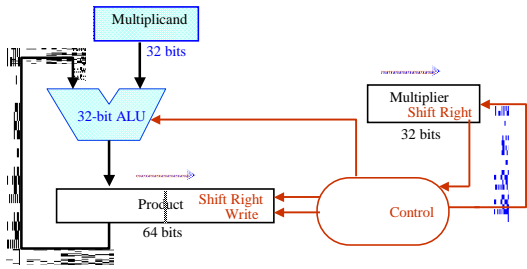- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg



Multiply Algorithm Version 2

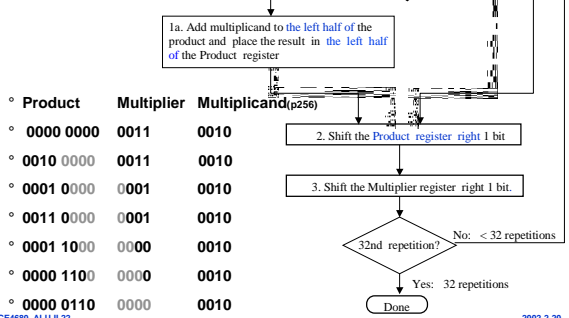- Addition performed only on left half of product register
- Shift of product Register





Observations on Multiply Version 2

- Product register wastes space that exactly matches size of multiplier => combine Multiplier register and Product register

MULTIPLY HARDWARE Version 3

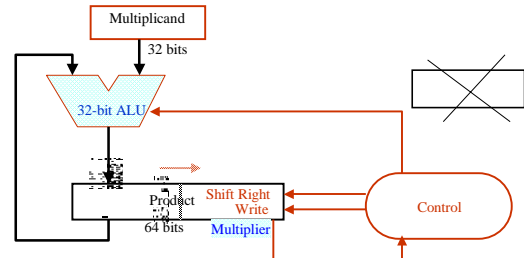- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



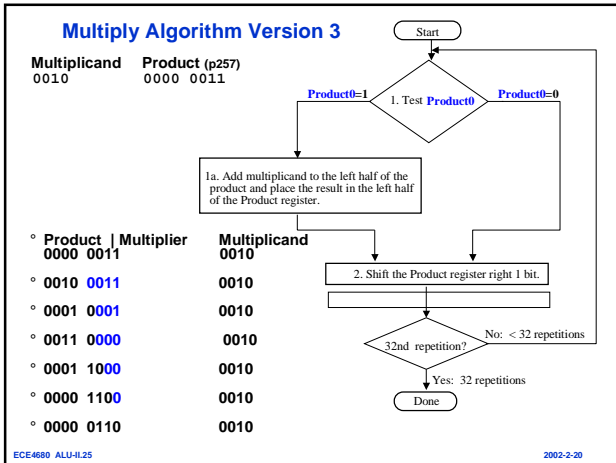

- ### Observations on Multiply Version 3
- 2 steps per bit because Multiplier & Product combined
 - MIPS registers Hi and Lo are left and right half of Product
 - Gives us MIPS instruction MultU
 - What about signed multiplication?
 - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
 - Booth's Algorithm is more elegant way to multiply signed numbers using same hardware as before
- ECE4680 ALU-HI.26 2002-2-20

Motivation for Booth's Algorithm

◦ Example $2 \times 6 = 0010 \times 0110$:

0010	
x 0110	
+ 0000	shift (0 in multiplier)
+ 0010	add (1 in multiplier)
+ 0100	add (1 in multiplier)
+ 0000	shift (0 in multiplier)

00011100	

◦ ALU with add or subtract gets same result in more than one way:

6 = -2 + 8, or

0110 = -0010 + 1000 = 1110 + 1000

◦ Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one. For example

0010	
x 0110	
+ 0000	shift (0 in multiplier)
- 0010	sub (first 1 in multiplier)
+ 0000	shift (middle of string of 1s)
+ 0010	add (prior step had last 1)

00001100	

ECE4680 ALU-HI.27 2002-2-20

Booth's Algorithm Insight

end of run middle of run beginning of run

0 1 1 1 1 0

Current Bit	Bit to the Right	Explanation	Example
1	0	Beginning of a run of 1s	000111 <u>1</u> 000
1	1	Middle of a run of 1s	000111 <u>1</u> 000
0	1	End of a run of 1s	000 <u>1</u> 111000
0	0	Middle of a run of 0s	000 <u>1</u> 111000

Originally for Speed since shift faster than add for his machine

◦ Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one

-1
+ 10000

01111

ECE4680 ALU-HI.28 2002-2-20

Booth's Algorithm

1. Depending on the current and previous bits, do one of the following:

- 00: Middle of a string of 0s, so no arithmetic operations.
- 01: End of a string of 1s, so add the multiplicand to the left half of the product.
- 10: Beginning of a string of 1s, so subtract the multiplicand from the left half of the product.
- 11: Middle of a string of 1s, so no arithmetic operation.

2. As in the previous algorithm, shift the Product register right (arith) 1 bit.

Multiplicand	Product (2 x 7)	Multiplicand	Product (2 x -3)
0010	0000 0111 0	0010	0000 1101 0

ECE4680 ALU-HI.29 2002-2-20

Booth's Example: 2 x 7 (p261)

Operation	Multiplicand	Product Multiplier	next?
0. initial value	0010	0000 0111 0	10 -> sub
1a. P = P - m	1110	+ 1110 1110 0111 0	shift P (sign ext)
1b.	0010	1111 0011 1	11 -> nop, shift
2.	0010	1111 1001 1	11 -> nop, shift
3.	0010	1111 1100 1	01 -> add
4a.	0010	+ 0010 0001 1100 1	shift
4b.	0010	0000 1110 0	done

mythical bit

ECE4680 ALU-HI.30 2002-2-20

Booths Example: 2×-3 (pp261-262)

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 1101 0	10 -> sub
1a. $P = P - m$	1110	+ 1110 1110 1101 0	shift P (sign ext)
1b.	0010	1111 0110 1 + 0010	01 -> add
2a.		0001 0110 1	shift P
2b.	0010	0000 1011 0 + 1110	10 -> sub
3a.	0010	1110 1011 0	shift
3b.	0010	1111 0101 1	11 -> nop
4a		1111 0101 1	shift
4b.	0010	1111 1010 1	done

mythical bit

Summary

- Instruction Set drives the ALU design
- Shifter: success refinement from 1/bit at a time shift register to barrel shifter
- Multiply: successive refinement to see final design
 - 32-bit Adder, 64-bit shift register, 32-bit Multiplicand Register
 - Booth's algorithm to handle signed multiplies
- There are algorithms that calculate many bits of multiply per cycle
- What's Missing from MIPS is Divide & Floating Point Arithmetic: Next time the Pentium Bug