

DIGITAL HARDWARE ARITHMETIC

CS 2600

The Two's Complement Representation

- ◆ Range of numbers in two's complement method:

$$-2^{n-1} \leq X \leq 2^{n-1} - 1$$


- ◆ Slightly asymmetric - one more negative number

- ◆ -2^{n-1} (represented by 10...0) does not have a positive equivalent

- ◆ A complement operation for this number will result in an overflow indication

- ◆ There is a unique representation for 0
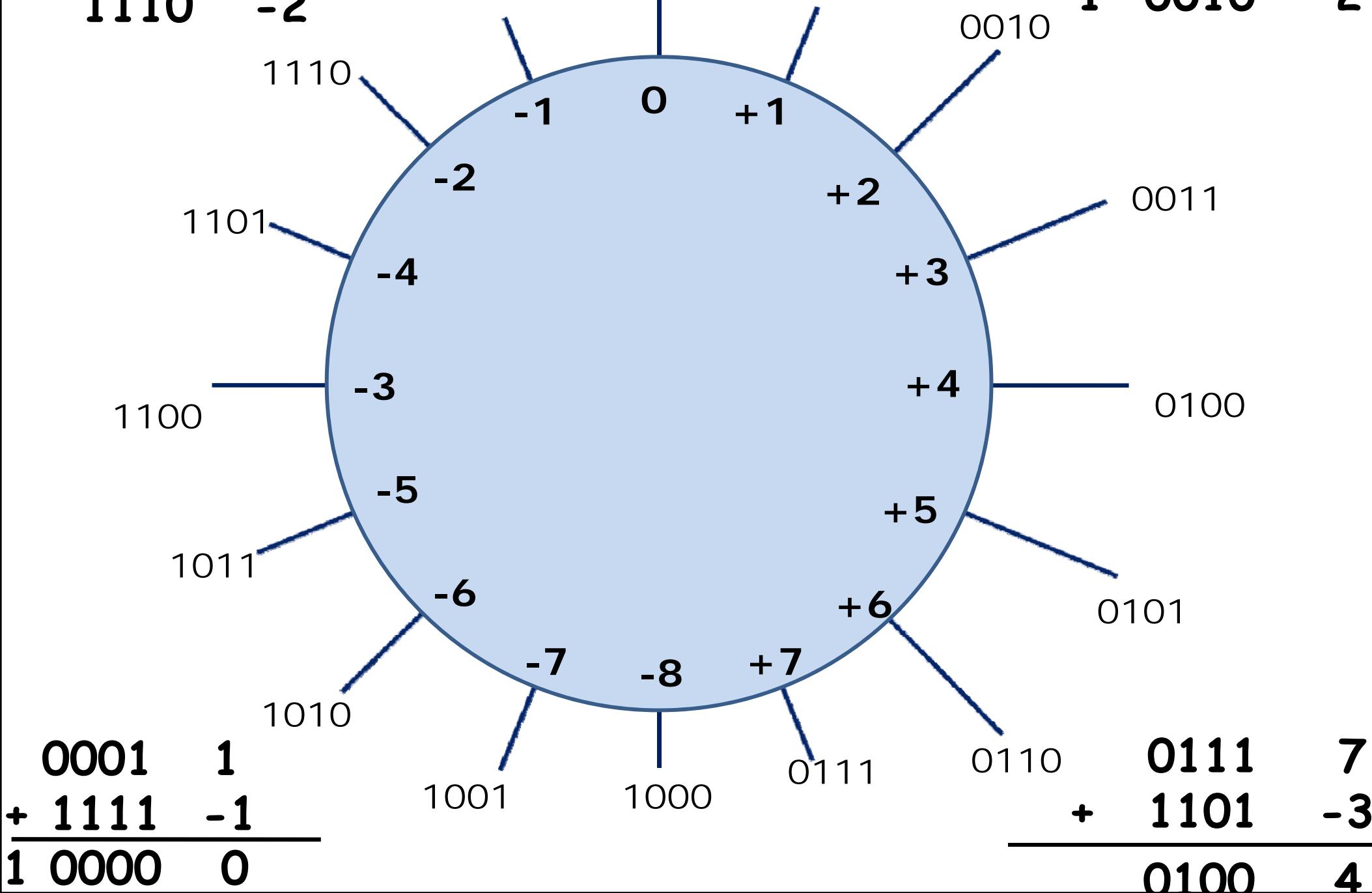
$$\begin{array}{r}
 0011 \quad 3 \\
 + 1011 \quad -5 \\
 \hline
 1110 \quad -2
 \end{array}
 \qquad
 \begin{array}{r}
 0101 \quad 5 \\
 + 1101 \quad -3 \\
 \hline
 1 \quad 0010 \quad 2
 \end{array}$$



- Example - (two's complement)

$$\begin{array}{r}
 01001 \quad 9 \\
 11001 \quad -7 \\
 \hline
 1\ 00010 \quad 2
 \end{array}$$

- Carry-out discarded - does not indicate overflow
- In general, if X and Y have opposite signs - no overflow can occur regardless of whether there is a carry-out or not

2's comp. binary	decimal
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7

No carry-out

$$\begin{array}{r}
 0\ 0\ 1\ 0\ 1\ 5 \\
 + 1\ 0\ 1\ 1\ 0\ -10 \\
 \hline
 1\ 1\ 0\ 1\ 1\ -5
 \end{array}$$

Carry-out

$$\begin{array}{r}
 0\ 1\ 0\ 1\ 0\ 10 \\
 + 1\ 1\ 0\ 1\ 1\ -5 \\
 \hline
 1\ 0\ 0\ 1\ 0\ 1\ 5
 \end{array}$$

◆ If X and Y have the same sign and result has different sign - overflow occurs

◆ Examples - (two's complement)

$$\begin{array}{r} 10111 \quad -9 \\ 10111 \quad -9 \\ \hline 1 \ 01110 \quad 14 = -18 \text{ mod } 32 \end{array}$$

* Carry-out and overflow

$$\begin{array}{r} 01001 \quad 9 \\ 00111 \quad 7 \\ \hline 0 \ 10000 \quad -16 = 16 \text{ mod } 32 \end{array}$$

* No carry-out but overflow

$$\begin{array}{r}
 0101 \quad 5 \\
 + 0011 \quad 3 \\
 \hline
 1000 \quad -8
 \end{array}$$

* No carry-out but overflow
 -> $8 \bmod 16$

$$\begin{array}{r}
 1011 \quad -5 \\
 + 1100 \quad -4 \\
 \hline
 1\ 0111 \quad 7
 \end{array}$$

* Carry-out and overflow
 → $-9 \bmod 16$

Condition for overflow (for logic implementation):

$S \text{ or } C \neq (MSB(A) = MSB(B));$


Full adder

$$\diamond S_i = X_i \oplus Y_i \oplus C_i \quad T_D = 1 \text{ (or 2);}$$

$$\diamond C_{i+1} = X_i \cdot Y_i + C_i \cdot (X_i + Y_i) \quad T_D = 2;$$

Assume 3-i/p XOR gate for S_i and SOP form for C_{i+1}

Ripple-Carry Adder

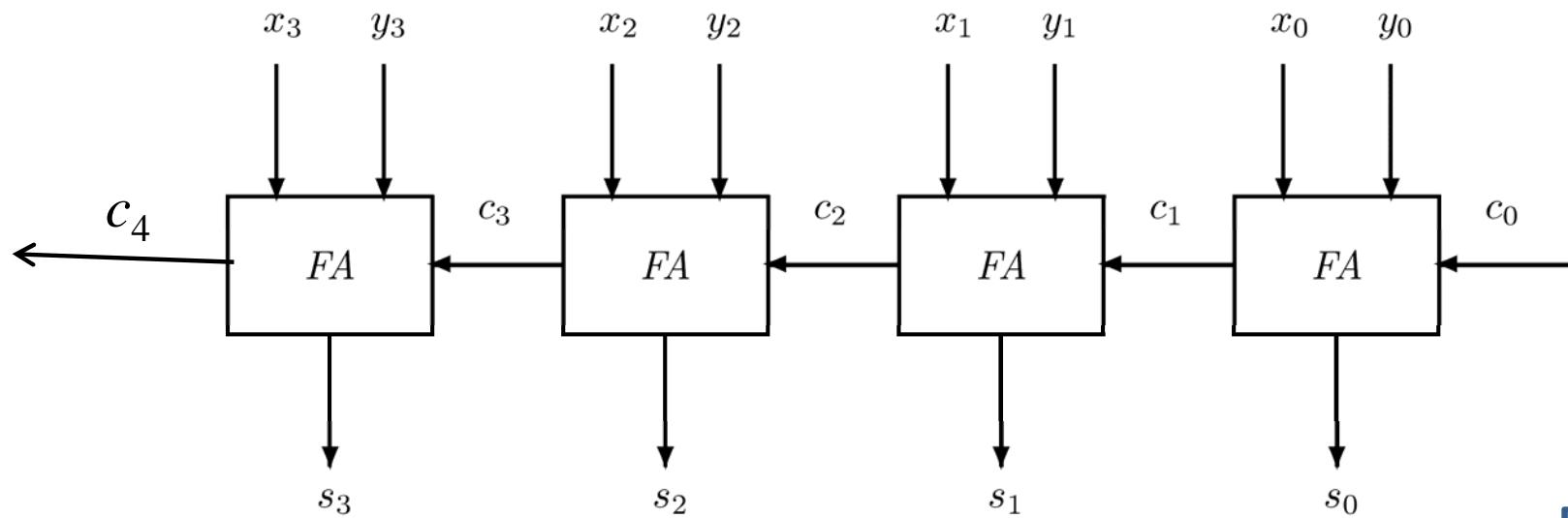

$$O = C_n \oplus C_{n-1};$$

$$O = x_{n-1} y_{n-1} \bar{S}_{n-1} + \bar{x}_{n-1} \bar{y}_{n-1} \bar{S}_{n-1}$$

$$T_{D/C} =$$

$$T_{D/S} =$$

$$T_{D/O} =$$

Subtraction

- ◆ Subtract operation, $X-Y$, is performed by adding the complement of Y to X
- ◆ In the two's complement system -



$$X-Y = X + (\bar{Y}+1)$$

- ◆ This still requires only a single adder operation, since 1 is added through the forced carry input to the binary adder

Use EX_OR to produce complement (use one I/P bit as flag):
- Show how ??
- draw Ckt.

◆ $S_i = X_i \oplus Y_i \oplus C_i$

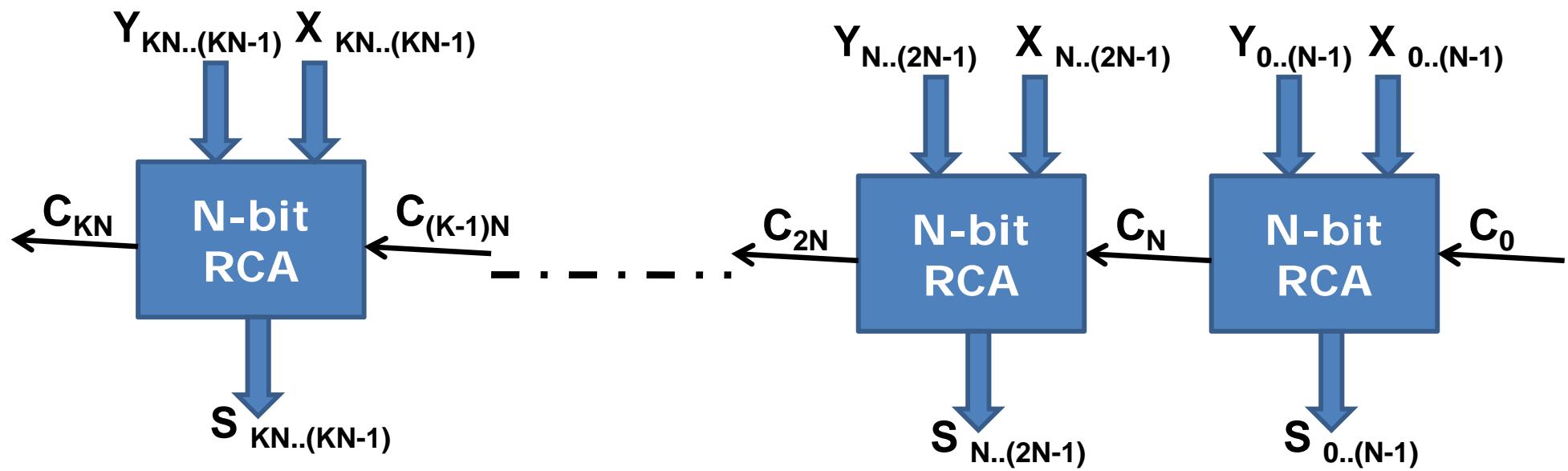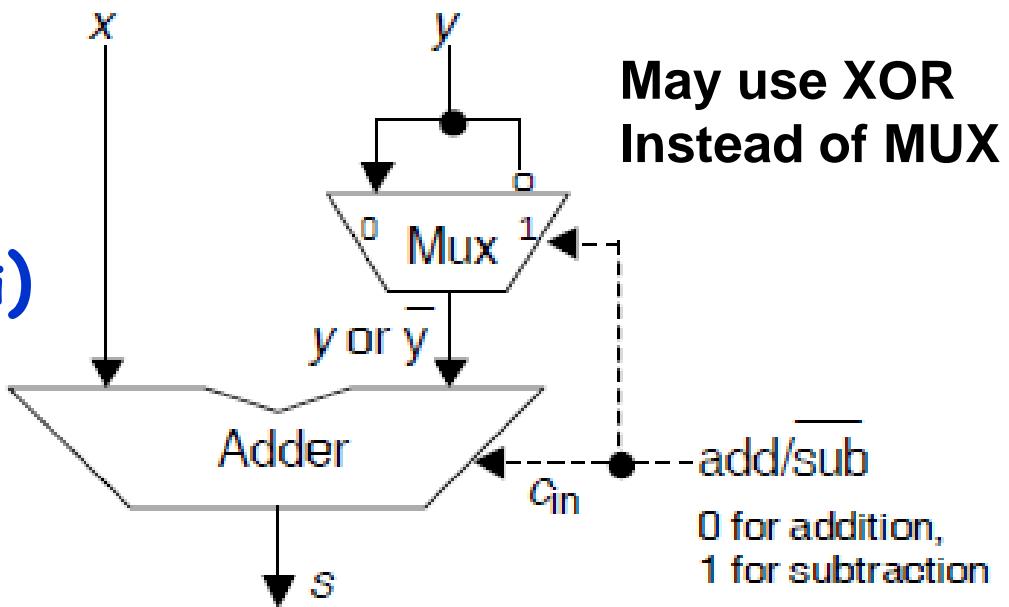◆ $C_{i+1} = X_i \cdot Y_i + C_i \cdot (X_i + Y_i)$




Cascade of K N-bit RCAs also possible – but delay is large

Look-Ahead Adder

Let $P_i = x_i \oplus y_i, G_i = x_i y_i$;

$$S_i = P_i \oplus C_i$$


$$c_{i+1} = G_i + P_i C_i$$

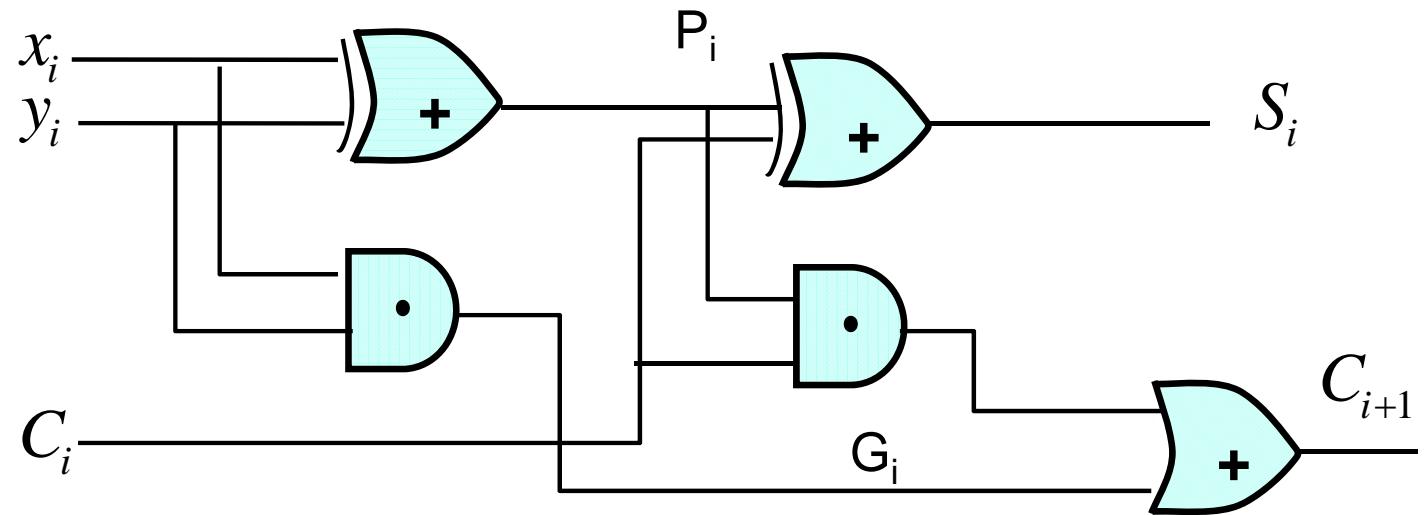

G_i and P_i are termed:

Carry Generate and Carry Propagate

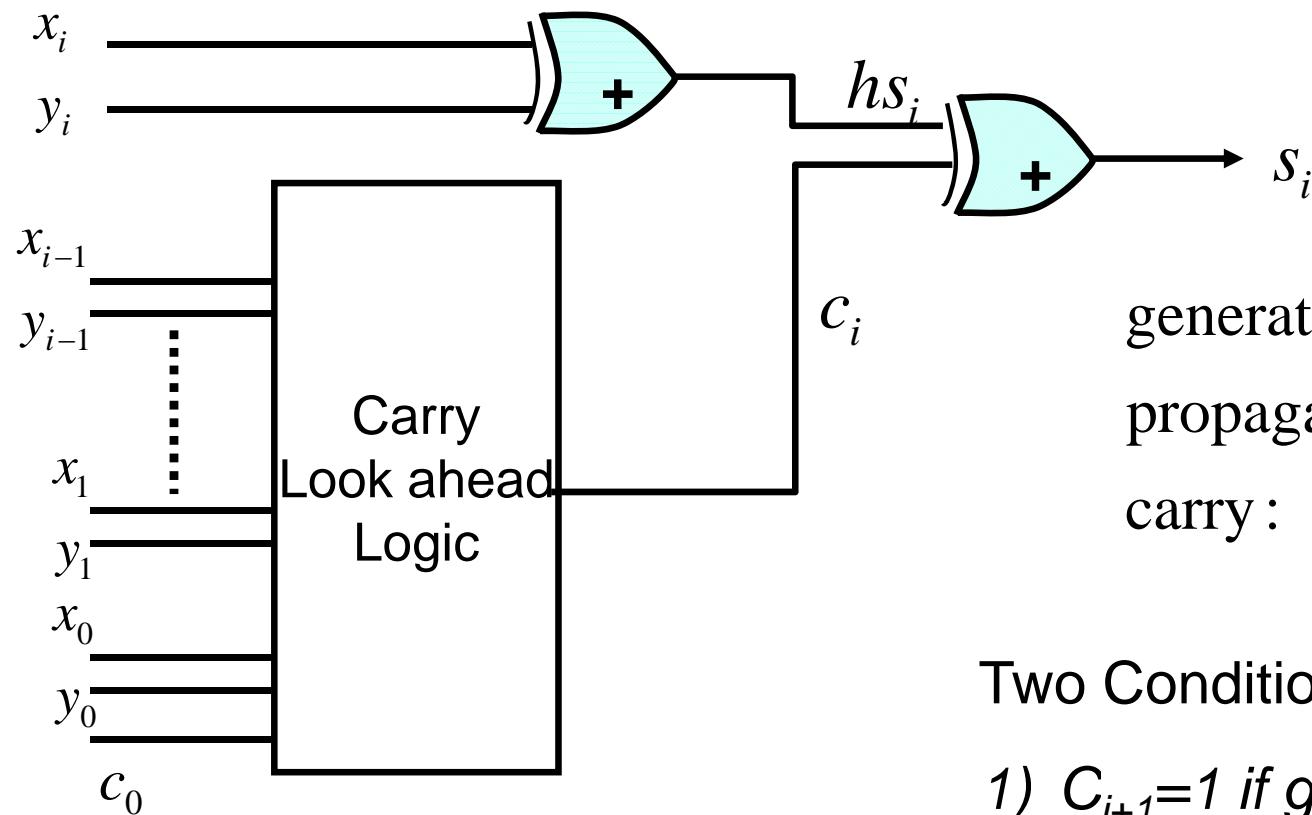Examples: 74283 - a 4-bit binary full adder with fast carry



$$\text{generate: } g_i = x_i y_i$$

$$\text{propagate: } p_i = x_i + y_i$$

$$\text{carry: } c_{i+1} = g_i + p_i c_i$$

Two Conditions:

$$1) C_{i+1}=1 \text{ if } g_i=1$$

$$2) C_{i+1}=1 \text{ if } C_i=1 \text{ and } p_i=1$$

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

74283 – contd.

$$hs_i = x_i \oplus y_i = (x_i + y_i)(\overline{x_i \cdot y_i}) = p_i \overline{g}_i$$

$$c_{i+1} = g_i(p_i) + p_i c_i \quad \text{i.e. when } g_i=1, p_i=1$$

$$= p_i(g_i + c_i)$$

$$c_1 = p_0(g_0 + c_0)$$

$$\begin{aligned} c_2 &= p_1(g_1 + c_1) = p_1(g_1 + p_0(g_0 + c_0)) \\ &= p_1(g_1 + p_0)(g_1 + g_0 + c_0) \end{aligned}$$

$$c_3 = p_2(g_2 + c_2)$$

$$= p_2(g_2 + p_1)(g_2 + g_1 + p_0)(g_2 + g_1 + g_0 + p_0)$$

$$c_4 = p_3(g_3 + p_2)(g_3 + g_2 + p_1)$$

$$(g_3 + g_2 + g_1 + p_0)(g_3 + g_2 + g_1 + g_0 + c_0)$$

Carry-Look-Ahead - FAST Adders

- ◆ $G_i = X_i Y_i$ - generated carry ;
- ◆ $P_i = X_i + Y_i$ - propagated carry
- ◆ $C_{i+1} = X_i Y_i + C_i (X_i + Y_i) = G_i + C_i P_i$

◆ Substituting

$$C_i = G_{i-1} + C_{i-1} P_{i-1}; \Rightarrow C_{i+1} = G_i + G_{i-1} P_i + C_{i-1} P_{i-1} P_i$$

◆ Further substitutions -

$$\begin{aligned} C_{i+1} &= G_i + G_{i-1} P_i + G_{i-2} P_{i-1} P_i + C_{i-2} P_{i-2} P_{i-1} P_i = \dots \\ &= G_i + G_{i-1} P_i + G_{i-2} P_{i-1} P_i + \dots + c_0 P_0 P_1 \dots P_i. \end{aligned}$$

◆ All carries can be calculated **in parallel**, using:

$X_{n-1}, X_{n-2}, \dots, X_0$, $Y_{n-1}, Y_{n-2}, \dots, Y_0$, and forced carry C_0



- ◆ Method called: “Carry Look Ahead or Propagation” for Fast Adder design

$$C_2 = G_1 + P_1 C_1$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 C_1$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 C_1$$

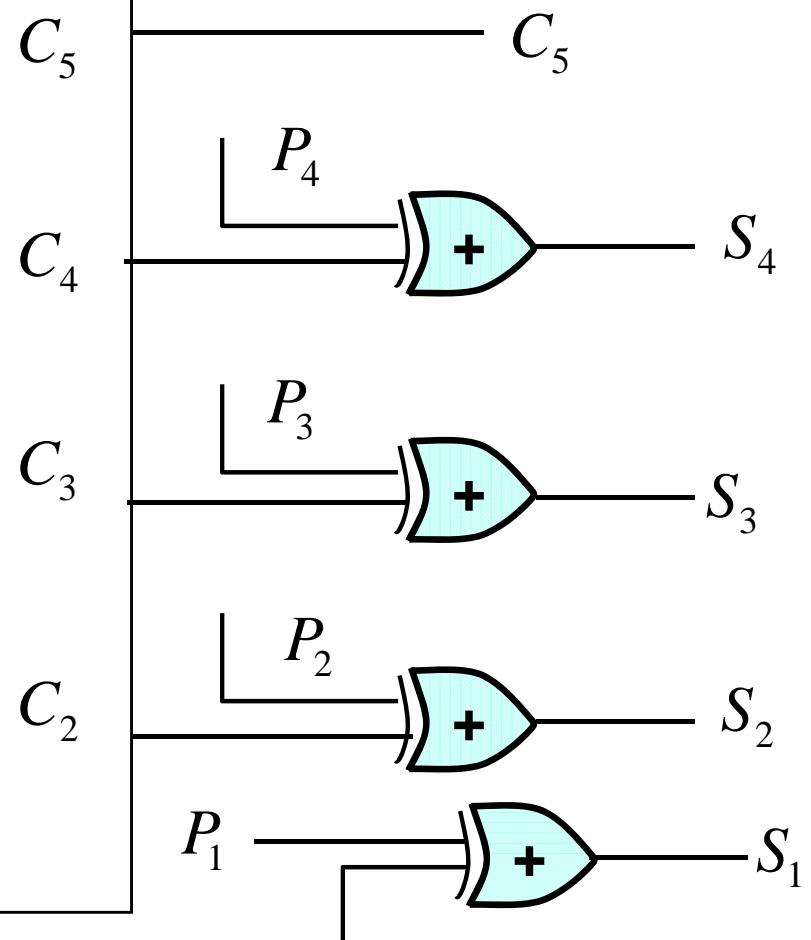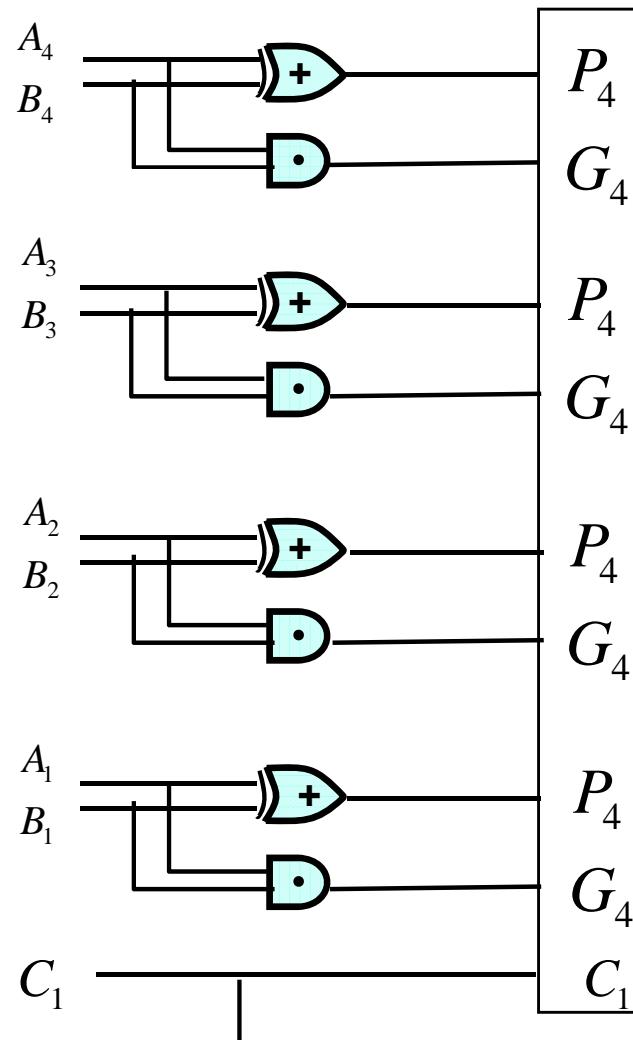**Compare overall delay,
w.r.t. previous circuits**



Example - 4-bit Adder

$$c_1 = G_0 + c_0 P_0,$$


$$c_2 = G_1 + G_0 P_1 + c_0 P_0 P_1,$$

$$c_3 = G_2 + G_1 P_2 + G_0 P_1 P_2 + c_0 P_0 P_1 P_2,$$

$$c_4 = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + c_0 P_0 P_1 P_2 P_3$$

- Draw Ckt.
- How many gates ?
- Delay: For C_i 's: $T_D = 3$; $S_i = 3 + 2 = 5$.

For RCA: $T_{D/RCA} = 8$;

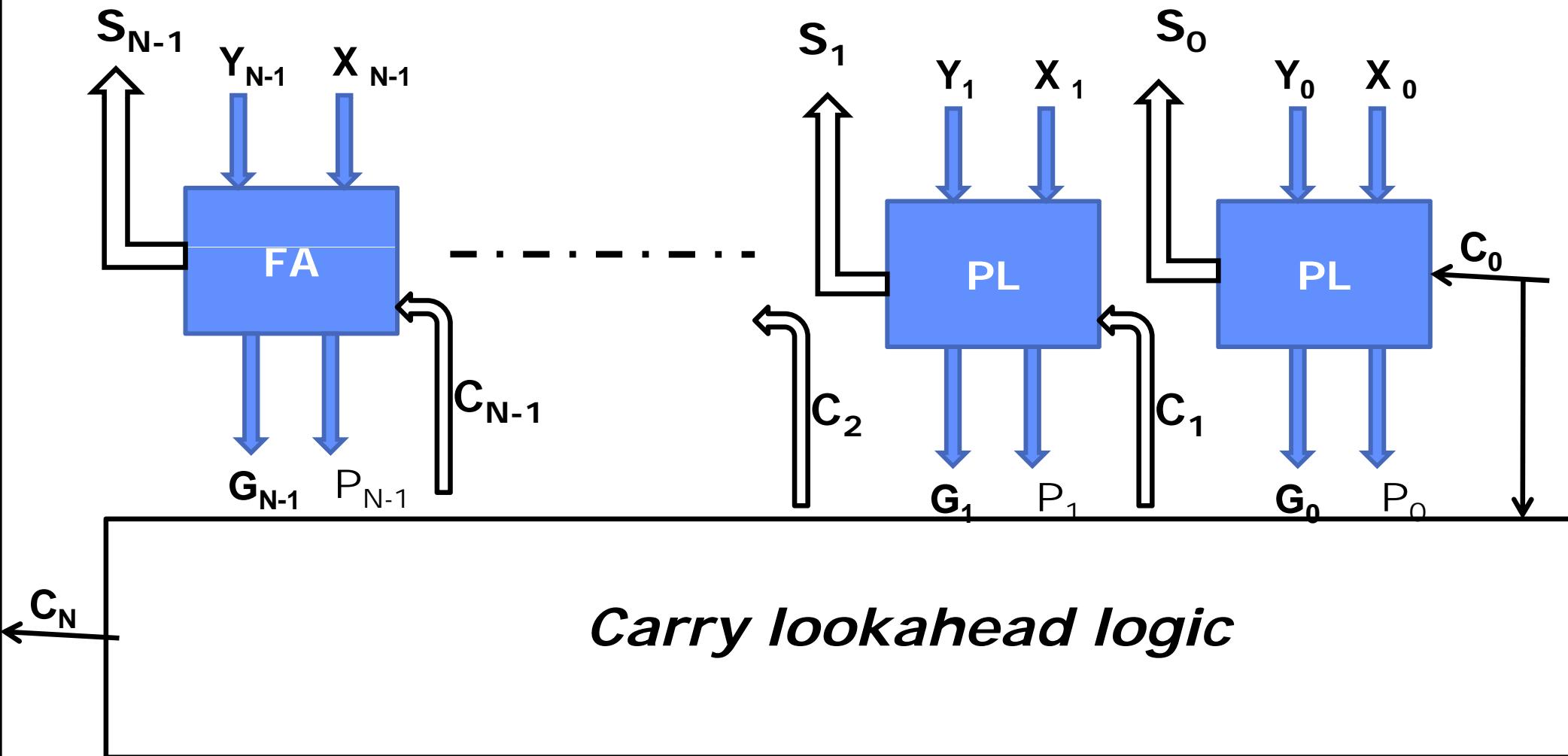


Carry lookahead Fast Adder

Delay of Carry-Look-Ahead Adders

- ◆ ΔG - delay of a single gate
- ◆ At each stage
 - * Delay of ΔG for generating all P_i and G_i
 - * Delay of $2\Delta G$ for generating all C_i (two-level gate implementation)
 - * Delay of $2\Delta G$ for generating sum digits S_i in parallel (two-level gate implementation)
 - * Total delay of $5\Delta G$ regardless of n - number of bits in each operand
- ◆ Large n ($=32$) - large number of gates with large fan-in
 - * Fan-in - number of gate inputs, $n+1$ here
- ◆ Span of look-ahead must be reduced at expense of speed

Reducing Span

- ◆ n stages divided into groups - separate carry-look-ahead in each group
- ◆ Groups interconnected by ripple-carry method
 - * Equal-sized groups - modularity - one circuit designed
 - * Commonly - group size **4** selected - $n/4$ groups
 - * **4** is factor of most word sizes
 - * Technology-dependent constraints (number of input/output pins)
 - * ICs adding two **4** digits sequences with carry-look-ahead exist
 - » ΔG needed to generate all **P_i** and **G_i**
 - » $2\Delta G$ needed to propagate a carry through a group once the **P_i, G_i, C₀** are available
 - » $(n/4)2\Delta G$ needed to propagate carry through all groups
 - » $2\Delta G$ needed to generate sum outputs
 - * Total - $(2(n/4)+3)\Delta G = ((n/2)+3)\Delta G$ - a reduction of almost 75% compared to $2n\Delta G$ in a ripple-carry adder

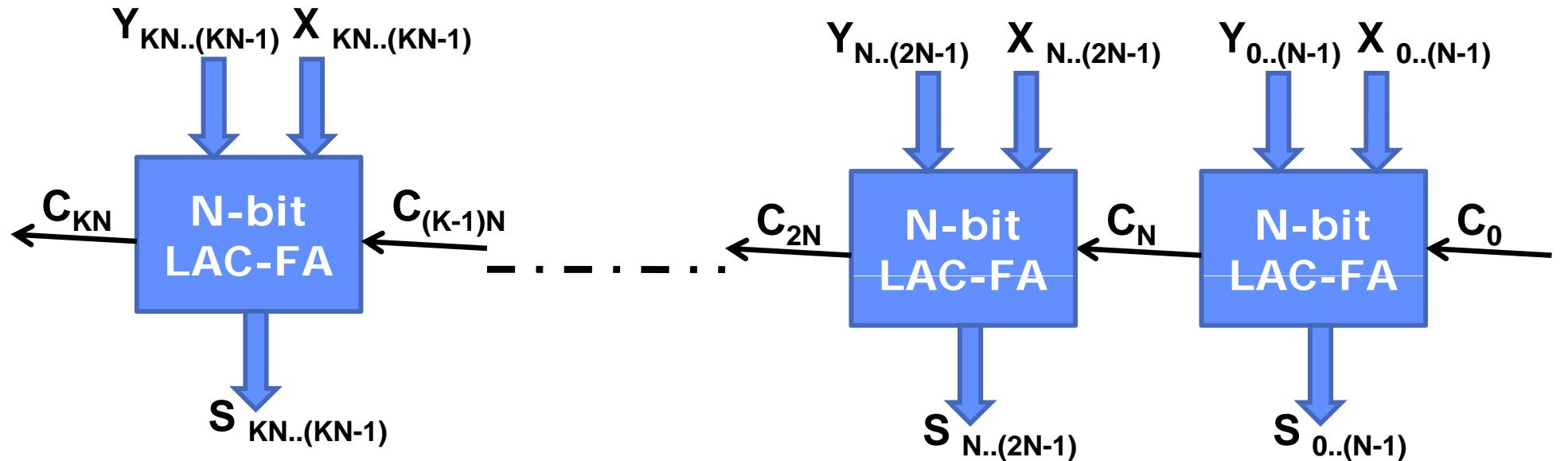

Cascade of K N-bit LAC-FAs also possible

Comparison of the Delay of different systems

Speed-up for higher level carry bits

$$c_1 = G_0 + c_0 P_0,$$

$$c_2 = G_1 + G_0 P_1 + c_0 P_0 P_1,$$

$$c_3 = G_2 + G_1 P_2 + G_0 P_1 P_2 + c_0 P_0 P_1 P_2,$$

$$c_4 = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + c_0 P_0 P_1 P_2 P_3$$

Let:

$$P_o^* = P_3 P_2 P_1 P_0; \quad G_o^* = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0;$$

$$\text{Then, } C_4 = G_o^* + P_o^* C_0$$


If:

$$P_1^* = P_7 P_6 P_5 P_4; \quad G_1^* = G_7 + P_7 G_6 + P_7 P_6 G_5 + P_7 P_6 P_5 G_4;$$

$$\text{Then, } C_8 = G_1^* + P_1^* C_4 = G_1^* + P_1^* G_0^* + P_1^* P_0^* C_0$$

$$\text{Similarly, } C_{12} = G_2^* + P_2^* C_8; \quad C_{16} = G_3^* + P_3^* C_{12}$$

16-bit 2-level Carry-look-ahead Adder

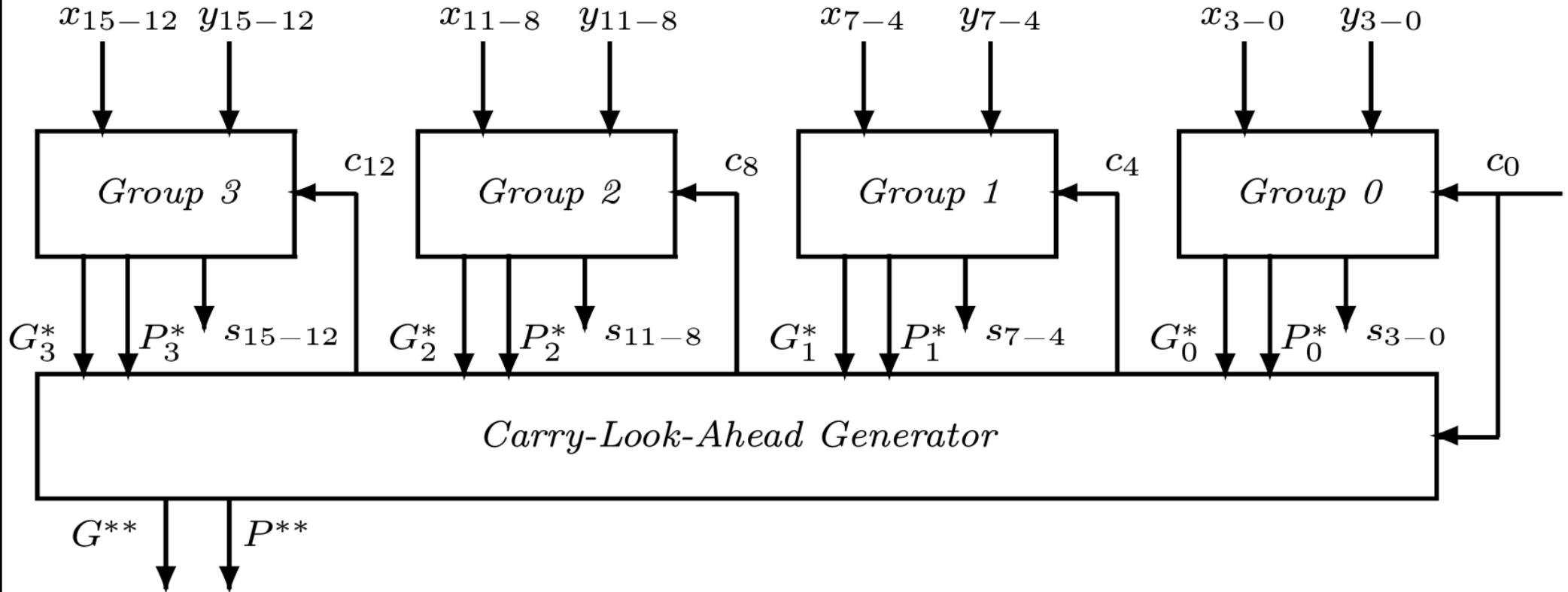

◆ **$n=16 - 4$ groups**

◆ **Outputs:** $G_o^*, G_1^*, G_2^*, G_3^*, P_0^*, P_1^*, P_2^*, P_3^*$;

◆ **Inputs to a carry-look-ahead generator with outputs C_4, C_8, C_{12}**

$$c_4 = G_0^* + c_0 P_0^*,$$

$$c_8 = G_1^* + G_0^* P_1^* + c_0 P_0^* P_1^*,$$

$$c_{12} = G_2^* + G_1^* P_2^* + G_0^* P_1^* P_2^* + c_0 P_0^* P_1^* P_2^*$$

$$C_4 = G_o^* + P_o^* C_0; \quad C_8 = G_1^* + P_1^* C_4 = G_1^* + P_1^* G_0^* + P_1^* P_0^* C_4$$

Similarly, $C_{12} = G_2^* + P_2^* C_8$

$$= G_2^* + P_2^* G_1^* + P_2^* P_1^* G_0^* + P_2^* P_1^* P_0^* C_0$$

$$C_{16} = G_3^* + P_3^* C_{12}$$

$$= G_3^* + P_3^* G_2^* + P_3^* P_2^* G_1^* + P_3^* P_2^* P_1^* G_0^* + P_3^* P_2^* P_1^* P_0^* C_0$$

Expression/Output (4-stage block)	Implementation Delay	Total Delay
$G_i; P_i$	1	1
$G_i^*; P_i^*$	2; 1	3; 2
$C_{i=4, 8, 12, 16}$	2	5
S_i	$2 + 1 = 3$	8


For LAC-L1, delays are: $C_{16} \rightarrow 9$, $S_{15} \rightarrow 10$

$$C_{12} \rightarrow C_{15} :$$

$$5 + 2 = 7;$$

$$S_{15} :$$

$$7 + 1 = 8$$

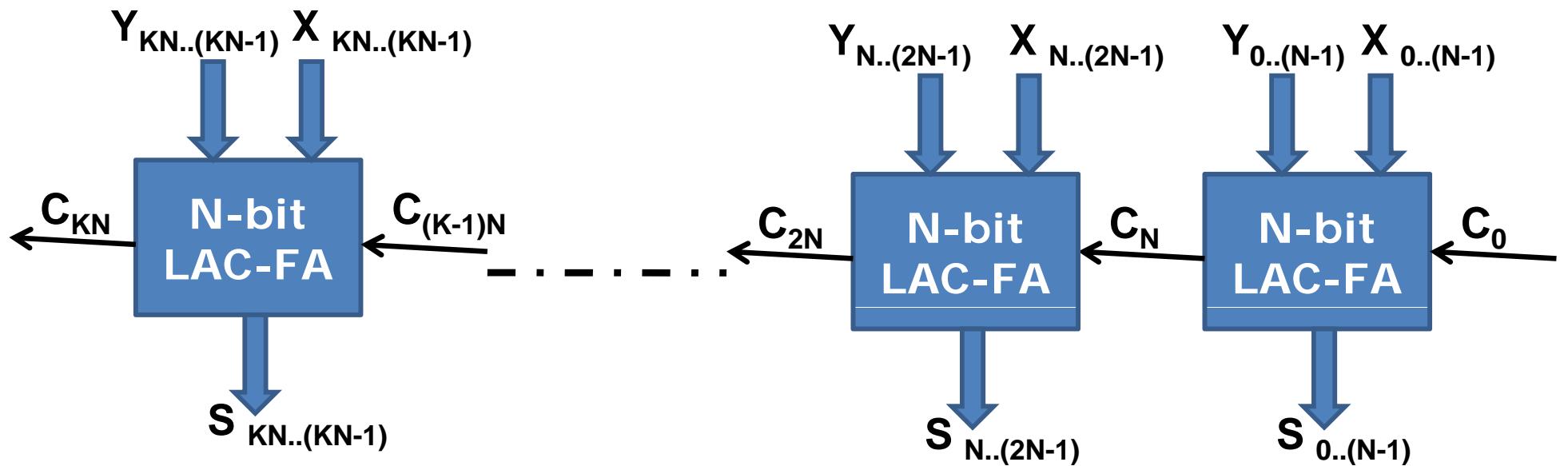

Cascade of K N(=16)-bit HLG&P-CAs also possible

$K = 2;$

Bit	Delay
$(K = 1) C_{16}$	5
$(K = 2) C_{28}, C_{32}$	$5 + 2 = 7$
$(K = 2) C_{28} \rightarrow C_{31}$	$7 + 2 = 9$
$(K = 2) S_{31}$	$9 + 1 = 10$

$K = 4;$

Bit	Delay
$(K = 2) C_{32}$	7
$(K = 3) C_{44}, C_{48}$	$7 + 2 = 9$
$(K = 4) C_{60}, C_{64}$	$9 + 2 = 11$
$(K = 4) C_{60} \rightarrow C_{63}$	$11 + 2 = 13$
$(K = 4) S_{63}$	$13 + 1 = 14$

Comparison of the Delay of different systems

Adder	C4	C8	C16	S15	C32	S31	C64	S63
RCA	8	16	32	31	64	63	128	127
LAC-FA	3	5	9	10	17	18	33	34
HLG&P-CA	-	-	5	8	7	10	11	14
??								

$$C_{16} = G_3^* + P_3^* C_{12}$$

L2 – HLG&P CA


$$= G_3^* + P_3^* G_2^* + P_3^* P_2^* G_1^* + P_3^* P_2^* P_1^* G_o^* + P_3^* P_2^* P_1^* P_0^* C_0$$

$$= G_o^{**} + P_0^{**} C_0;$$

where,

$$G_o^{**} = G_3^* + P_3^* G_2^* + P_3^* P_2^* G_1^* + P_3^* P_2^* P_1^* G_o^*;$$

$$P_0^{**} = P_3^* P_2^* P_1^* P_0^*$$

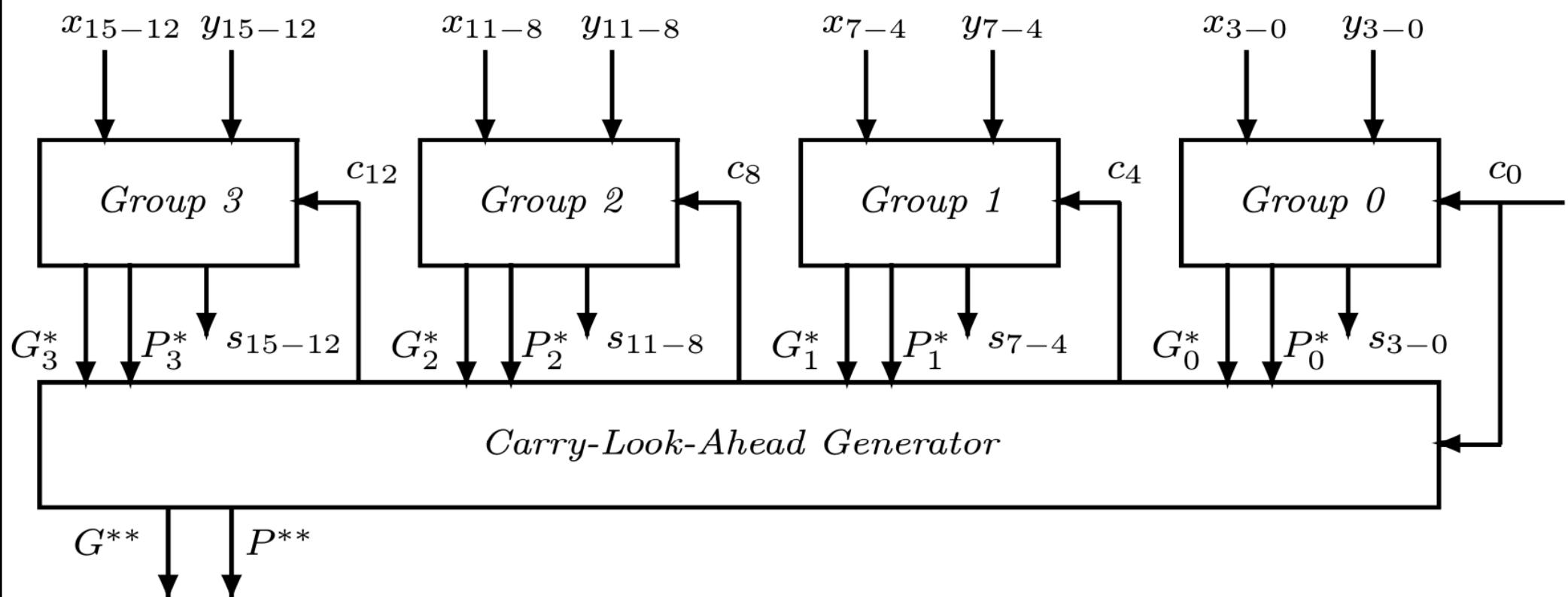

$$\begin{aligned}
 C_{16} &= G_3^* + P_3^* C_{12} \\
 &= G_3^* + P_3^* G_2^* + P_3^* P_2^* G_1^* + P_3^* P_2^* P_1^* G_o^* + P_3^* P_2^* P_1^* P_0^* C_0
 \end{aligned}$$

$$= G_o^{**} + P_0^{**} C_0;$$

where ,

Delay for C_{16} : 5

Delay for S_{63} : 12

Delay for C_{64} : 7

$$G_o^{**} = G_3^* + P_3^* G_2^* + P_3^* P_2^* G_1^* + P_3^* P_2^* P_1^* G_o^*;$$

$$P_0^{**} = P_3^* P_2^* P_1^* P_0^*$$

Comparison of the Delay of different FAST ADDER systems

Adder	C4	C8	C16	S15	C32	S31	C64	S63
RCA	8	16	32	31	64	63	128	127
LAC-FA	3	5	9	10	17	18	33	34
HLG&P-CA	-	-	5	8	7	10	11	14
2 nd LEVEL HLG&P-CA			5		7		7	12


Other Advanced Adders:

- Pipelined
- Manchester Adder
- Carry-Skip/Carry Select
- Parallel Prefix
- Carry-save adders – Wallace tree
-

MULTIPLIER UNIT

$$\begin{array}{r} 1101 \\ \times 1011 \\ \hline 1101 \\ 1101 \\ 0000 \\ 1101 \\ \hline 10011111 \end{array}$$

- ◆ Three types of high-speed multipliers:
- ◆ Sequential multiplier - generates partial products sequentially and adds each newly generated product to previously accumulated partial product
- ◆ Parallel multiplier - generates partial products in parallel, accumulates using a fast multi-operand adder
- ◆ Array multiplier - array of identical cells generating new partial products; accumulating them simultaneously

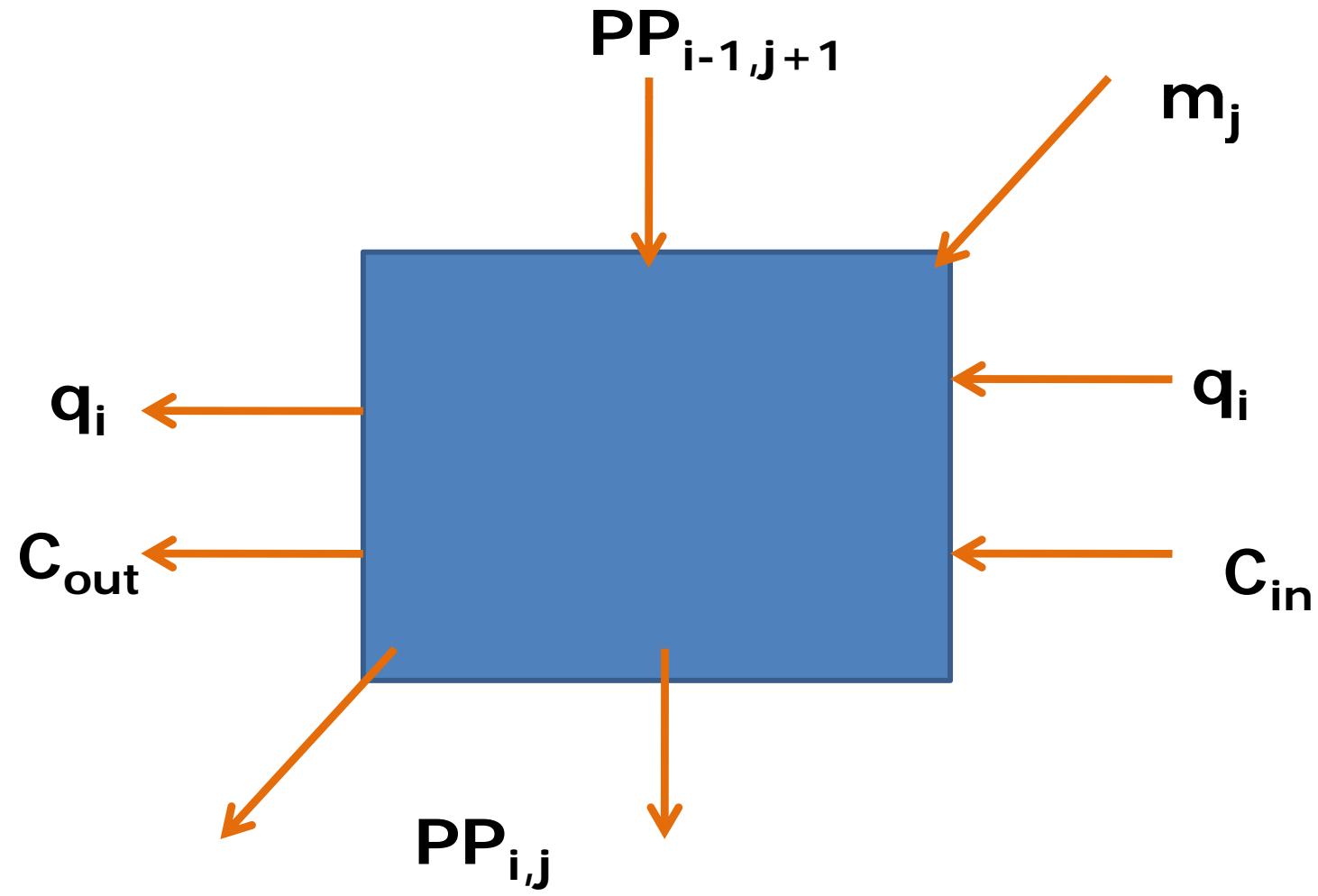

Typical Cell of an Array Multiplier

For Sequential circuit binary Multiplier:

Need - ADDER and Shift-right Registrar (SR) modules.

The control circuit requires a clock;

Multiplixer to decide:


- Add zero (only SR)

Or


- Add and shift (SR).

Result to be held in 2-K bit SR.

Unsigned Binary Multiplication

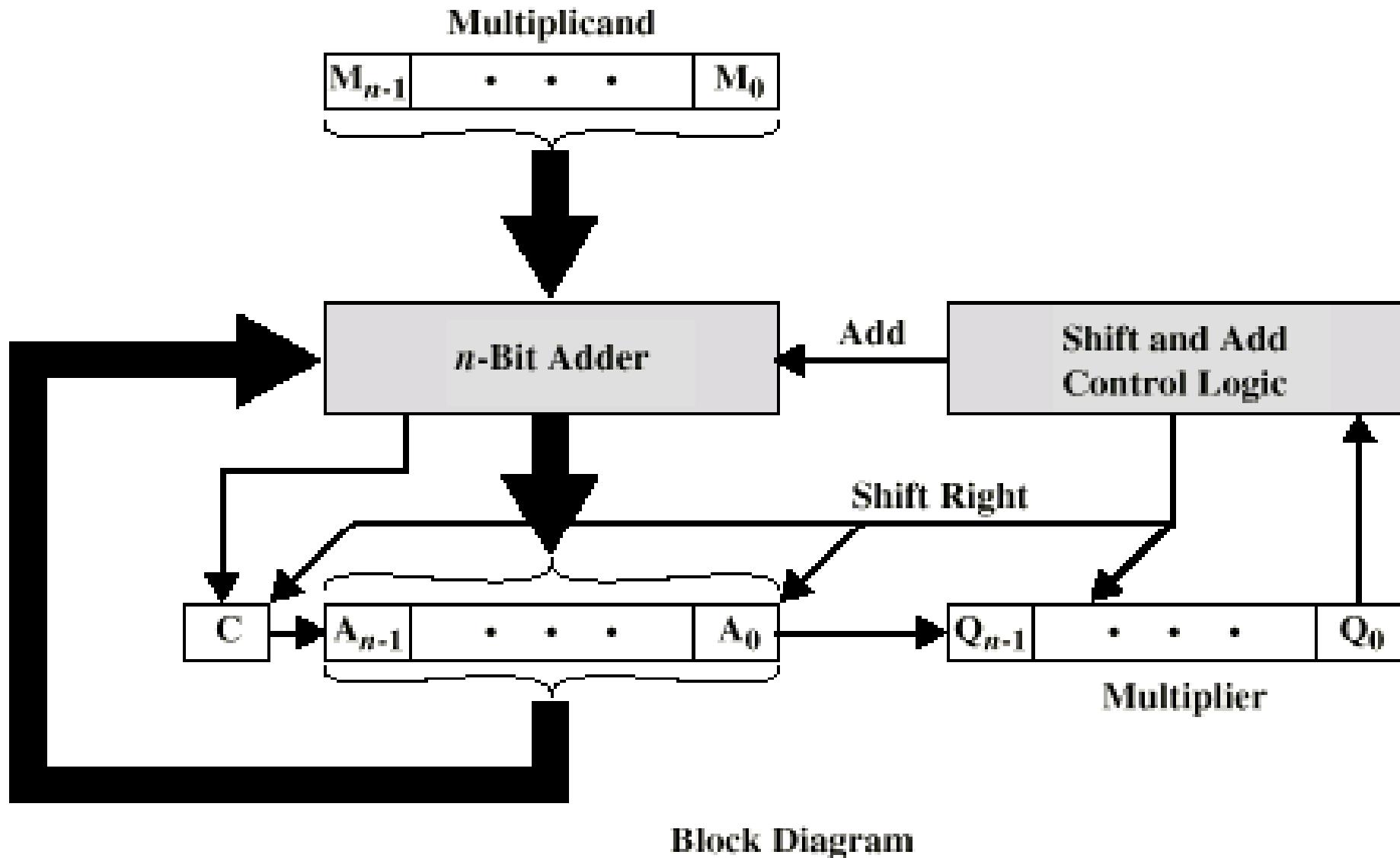

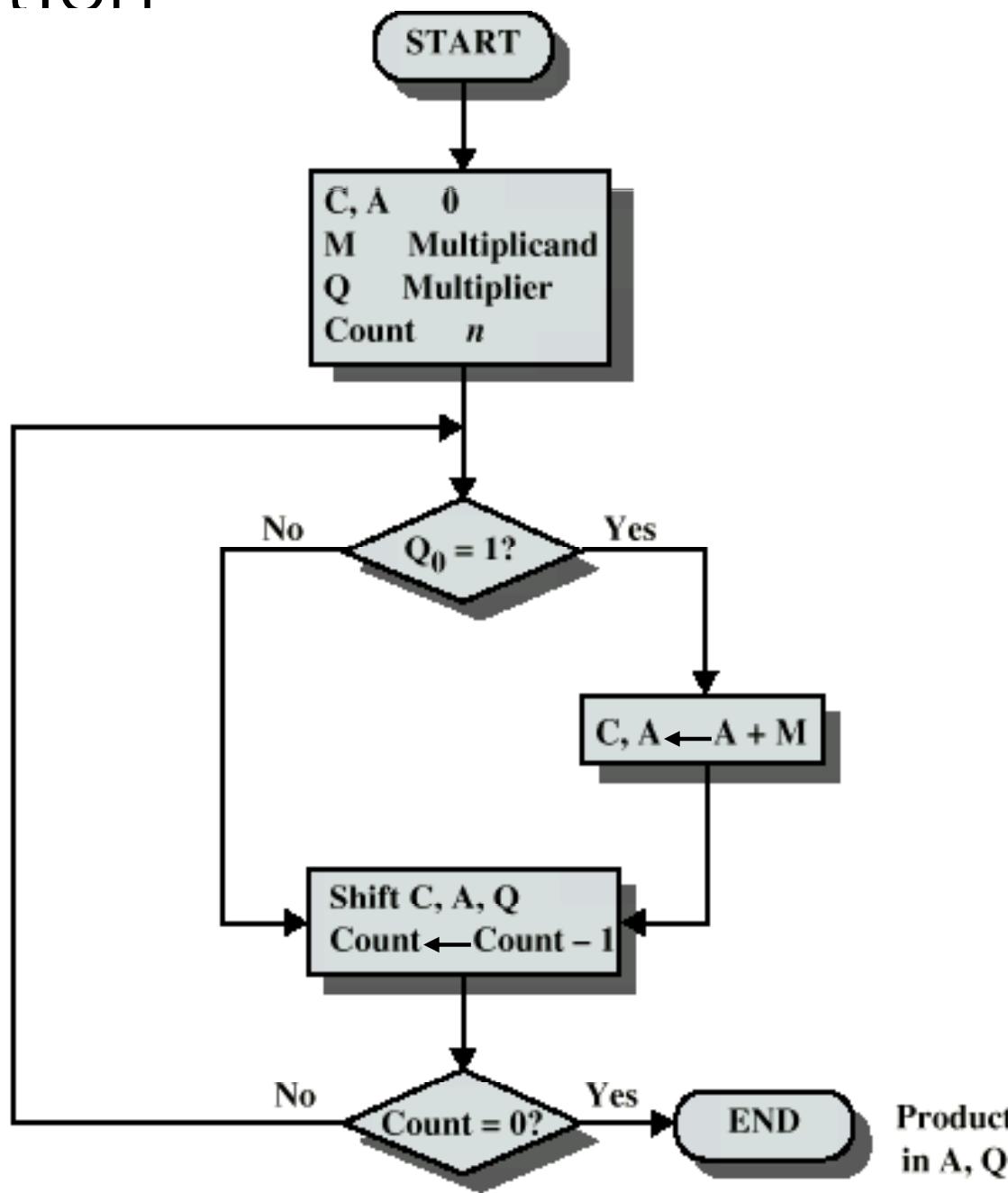Flowchart for Unsigned Binary Multiplication



Execution of Example

C	A	Q	M		
0	0000	1101	1011	Initial	values
0	1011	1101	1011	Add	} First
0	0101	1110	1011	Shift	} Cycle
0	0010	1111	1011	Shift	} Second
0	1101	1111	1011	Add	} Third
0	0110	1111	1011	Shift	} Cycle
1	0001	1111	1011	Add	} Fourth
0	1000	1111	1011	Shift	} Cycle

Booth's Algorithm for unsigned multiplication

Two basic principles:

- Strings of 0's require no addition – only shift
- String of 1's may be given special treatment:

001110 (+14) --> 010000 - 000010 (16 - 2);

1's from K-bit posn. to M-bit posn:

Treat as: $2^{K+1} - 2^M$;

In the above example K = 3, M = 1;

Thus M (Multiplicand) X 14 = M X 2^4 = M X 2^1 ;

Obtain result by:

M << 4 - M << 1 // view as C-code.

Take a example: multiplier = 30; Multiplicand = 45

(30) --> 32 - 2 =>

0011110 → 0100000 (32)
1111110 (-2)

Change Multiplier to:

0 (+1) 0 0 0 0 0
0 0 0 0 0 (-1) 0

								0	1	0	1	1	0	1
								0	+1	0	0	0	-1	0
								-	-	-	-	-	-	-
								0	0	0	0	0	0	0
1	1	1	1	1	1		0	1	0	0	1	1		
						0	0	0	0	0	0	0		
						0	0	0	0	0	0	0		
						0	0	0	0	0	0	0		
						0	1	0	1					
-	-	-	-	-	-	-	-	-	-	-	-	-	-	-
	0	0	1	0	1	0	1	0	0	0	1	1	0	

Good multiplier for coding:

0 0 0 0 0 1 1 1 1 1 1 1 0 0 0 0 1 1 1 1 1 1 0

Worst case multiplier:

0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0

Mult	0	0	1	0	1	1	0	0	1	1	1	0	1	0	1	1	0	0
Coded Mult.	0	+1	-1	+1	0	-1	0	+1	0	0	-1	+1	-1	+1	0	-1	0	0


Three rules for Booth's algm. implementation with operation on the multiplicand:

- For the LSB = 1 in a string of 1's in a multiplier:
Subtract the multiplicand from the partial product;
- For the first bit-0 (prior to a 1) in a string of 0's, the multiplicand is added to the partial product.
- For any pair of identical bit-pair in the mutliplier, the partial product is unchanged.

$$\begin{array}{ccccccc} 0 & 0 & 1 & 1 & 1 & 1 & 0 \rightarrow \\ 0 & +1 & 0 & 0 & 0 & -1 & 0 \end{array}$$

Multiplier Bits			
Bit i	Bit (i-1)		Opn. / Bit Pattern
0	0	$0 \times M$	Shift only; String of Zeros
0	1	$+1 \times M$	Add and Shift; End of a String of Ones
1	0	$-1 \times M$	Subtract and Shift; Beginning of a String of Ones
1	1	$0 \times M$	Shift only; String of Ones

Booth's Algorithm

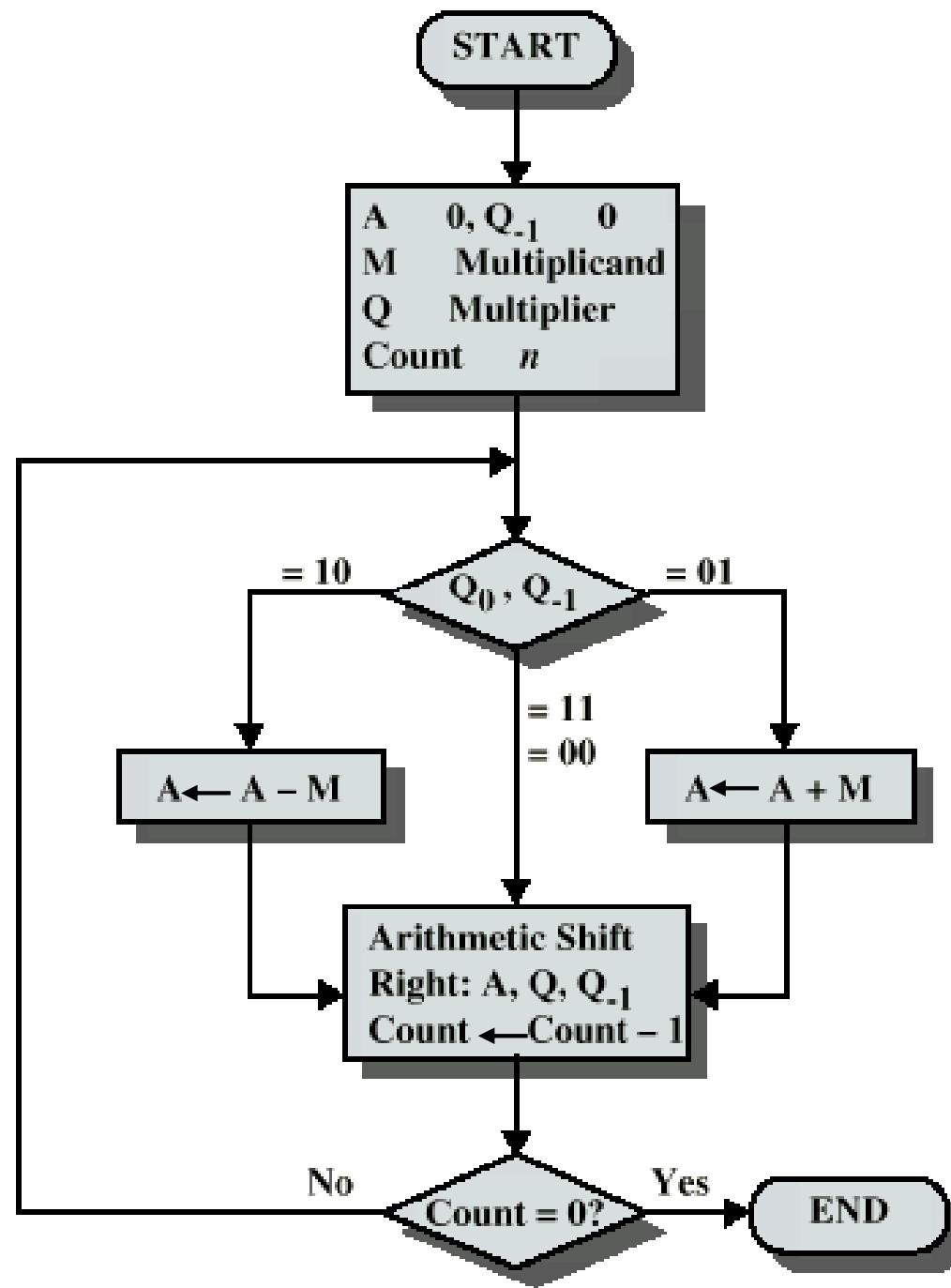

Example of Booth's Algorithm

A	Q	Q_{-1}	M	Initial Values	
0000	0011	0	0111		
1001	0011	0	0111	A	A - M } First
1100	1001	1	0111	Shift	Shift } Cycle
1110	0100	1	0111	Shift	Shift } Second Cycle
0101	0100	1	0111	A	A + M } Third
0010	1010	0	0111	Shift	Shift } Cycle
0001	0101	0	0111	Shift	Shift } Fourth Cycle

Execution of Example - Booth Multiplier

+13 → 01101

-6 → 11010 → 0 -1 +1 -1 0

								0	1	1	0	1
								0	-1	+1	-1	0
								-	-	-	-	-
								0	0	0	0	0
1	1	1	1	1	1	0	0	1	1	0	1	1
				0	0	0	1	1	0	1		
1	1	1	1	0	0	1	1					
0	0	0	0	0	0	0	0					
-	-	-	-	-	-	-	-	-	-	-	-	-
1	1	1	1	1	0	1	1	0	0	1	0	

Fast Multiplication done by:

- **Bit-pair recoding**
- **Carry-save Addition of Summands**
- + **Fast Look ahead Carry (with both above)**
- **Pipelined and Booth Array Tree**
- **etc.**

BIT-PAIR RECODING OF MULTIPLIERS

Observe this:

$$-6 \rightarrow 11010 \rightarrow 0 -1 \quad +1 \quad -1 \quad 0$$

Consider the pair of (+1, -1):

$$\Rightarrow (+1, -1) * M = 2xM - M = M$$

$$\Rightarrow (0, +1) * M;$$

Thus: $(+1, -1) == (0, +1)$;


which is also independent of the bit position "i".

Booth Pair	Equiv. to	Recoded pair
(+1, 0)	→	(0, +2)
(-1, +1)	→	(0, -1)
(0, 0)	→	(0, 0)
(0, 1)	→	(0, 1)
(+1, 1)	→	--
(-1, 0)	→	(0, -2)

BIT-PAIR RECODING OF MULTIPLIERS

Multiplier Bits		
Bit i	Bit (i-1)	
0	0	$0 \times M$
0	1	$+1 \times M$
1	0	$-1 \times M$
1	1	$0 \times M$

Booth Pair	Equiv. to	Recoded pair
(+1, 0)	→	(0, +2)
(-1, +1)	→	(0, -1)
(0, 0)	→	(0, 0)
(0, 1)	→	(0, 1)
(+1, 1)	→	--
(+1, -1)	→	(0, +1)
(-1, 0)	→	(0, -2)

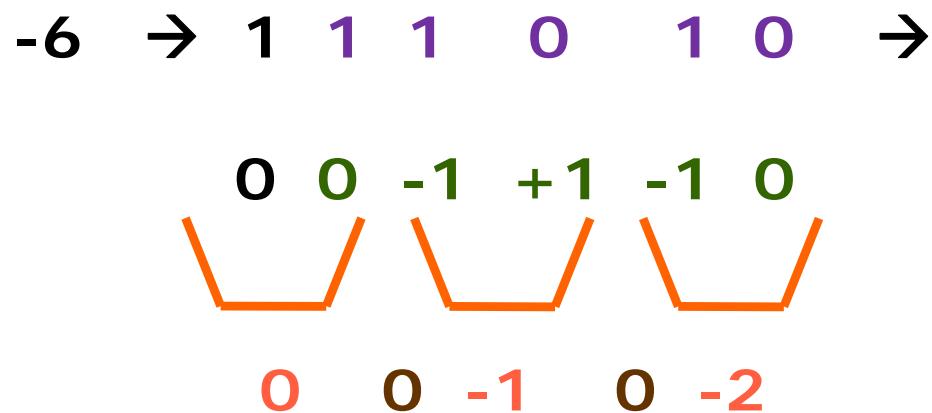

Execution of Example – Booth's Recoded Multiplier

+13 → 01101

-6 → 11010 → 0 -1 +1 -1 0 → 0 0 -1 0 -2

+13 → 01101; +26 → 011010; -26 → 100110;
-13 → 10011;

								0	1	1	0	1
								0	0	-1	0	-2
			-	-	-	-	-	-	-	-	-	-
	1	1	1	1	1	1	0	0	1	1	0	
	0	0	0	0	0	0	0	0	0	0	0	
	1	1	1	1	1	0	0	1	1			
	0	0	0	0	0	0	0	0				
	0	0	0	0	0	0	0					
-	-	-	-	-	-	-	-	-	-	-	-	-
1	1	1	1	1	0	1	1	0	0	1	0	


Unsigned Binary Division

		03																		
63)	243																		
	-	189																		
		54																		
			1	1	0	1	$\sqrt{ }$	1	0	0	0	1	0	0	1	1	0	1	0	1
		21																		
13)	274																		
	-	26																		
		14																		
		- 13																		
			01																	


+13 → 1101 ← DIVISOR;

274 → 100010010 ← DIVIDEND

Unsigned Binary Division

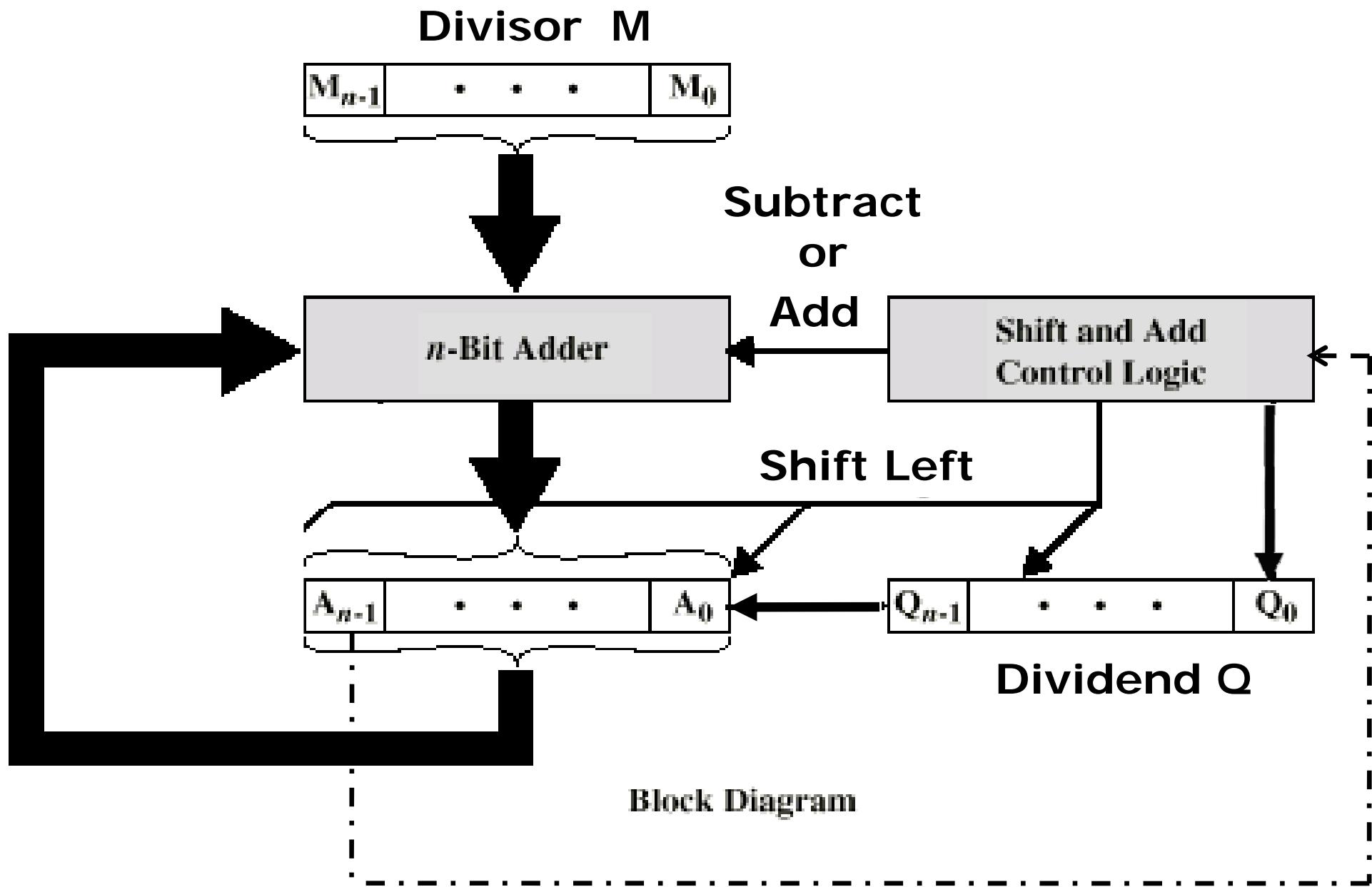

Flowchart for Unsigned Binary Division

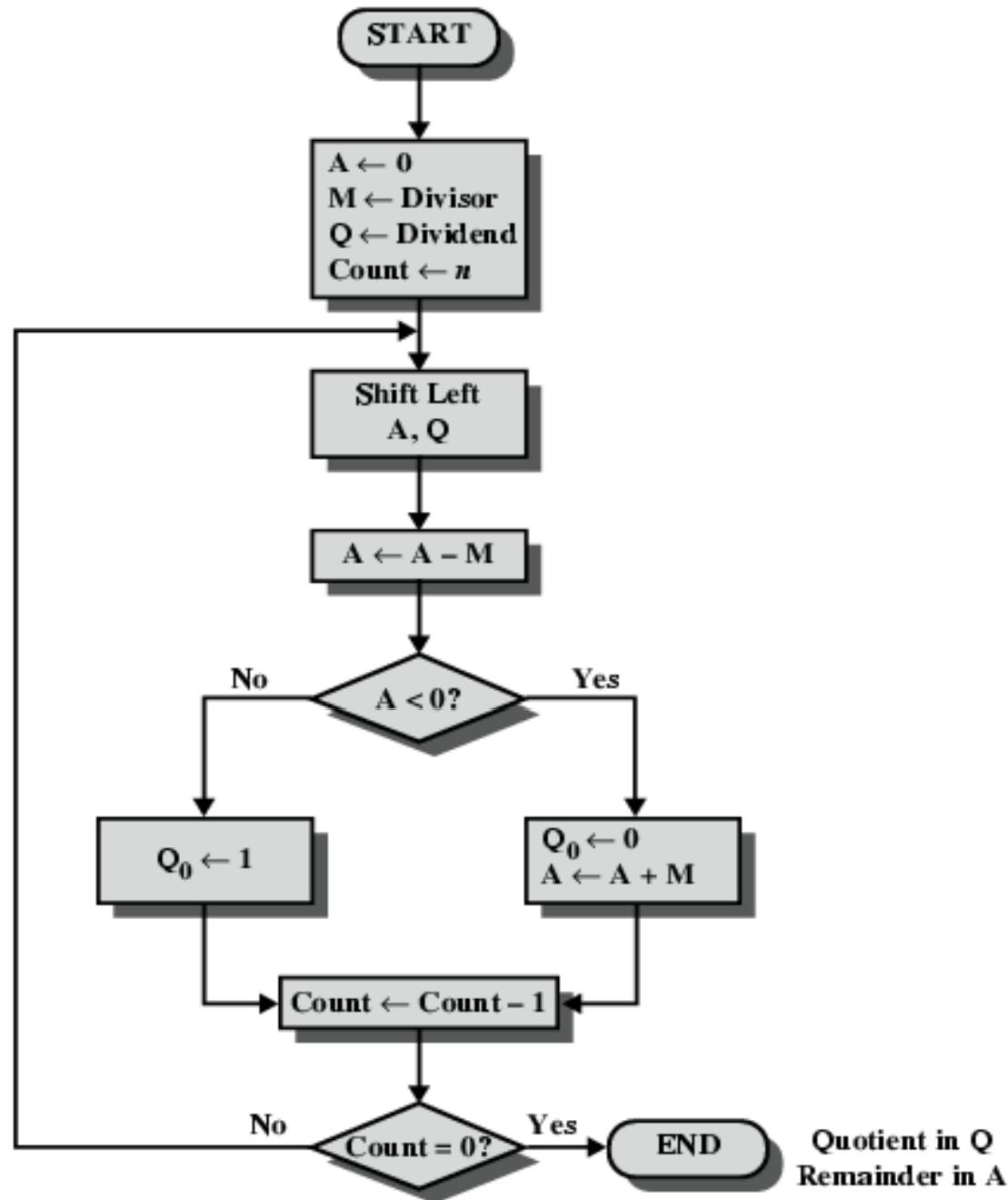

ALGO. for RESTORING DIVISION

Load Divisor in Reg. M;
Load Dividend in Reg. Q;
Set Reg. A = 0;

Repeat n times:

- Shift (left) A & Q (one bit posn.)
- $A = A - M;$
- If $\text{sgn}(A) == 1$ (-ve A)
 - Set $Q_0 = 0;$
 - $A = A + M;$

Else

- Set $Q_0 = 1;$

ANS:

End

- Quotient is in Reg. Q;
- Rem. is in Reg. A.

Dividend,
Q = 1000;

Divisor,
M = 11.

- M =
11101

Result, in
decimal ??

Quotient
= 02 ;

Rem = 02.

OPN.		REG. A					REG. Q			
INIT.		0	0	0	0	0	1	0	0	0
I	S. L.	0	0	0	0	1	0	0	0	
	Sub	1	1	1	1	0				
	Rstr	0	0	0	0	1	0	0	0	0
II	S. L.	0	0	0	1	0	0	0	0	
	Sub	1	1	1	1	1				
	Rstr	0	0	0	1	0	0	0	0	0
III	S. L.	0	0	1	0	0	0	0	0	
	Sub	0	0	0	0	1				
	Set-Q ₀	0	0	0	0	1	0	0	0	1
IV	S. L.	0	0	0	1	0	0	0	1	
	Sub	1	1	1	1	1				
	Rstr	0	0	0	1	0				0
Final Result		0	0	0	1	0	0	0	1	0
		REM					Q			

How to improve the Algo. ??

Repeat n times:

If A is +ve,

Opsns. :

- S.L. (A);

- Subtract M;

→ $(2A - M)$

- Shift (left) A & Q (one bit posn.)

- $A = A - M;$

- If $\text{sgn}(A) == 1$ (-ve A)

- Set $Q_0 = 0;$

- $A = A + M;$

Else

- Set $Q_0 = 1;$

End

If A is -ve,
Opsns. :

- $A + M$

- S.L. ($A+M$);

- Subtract M;

→ $(2A + 2M) - M$


= $2A + M$

How to improve the Algo. ??

If A is +ve,
Opns. :

- S.L. (A);
- Subtract M;

$$\rightarrow (2A - M)$$

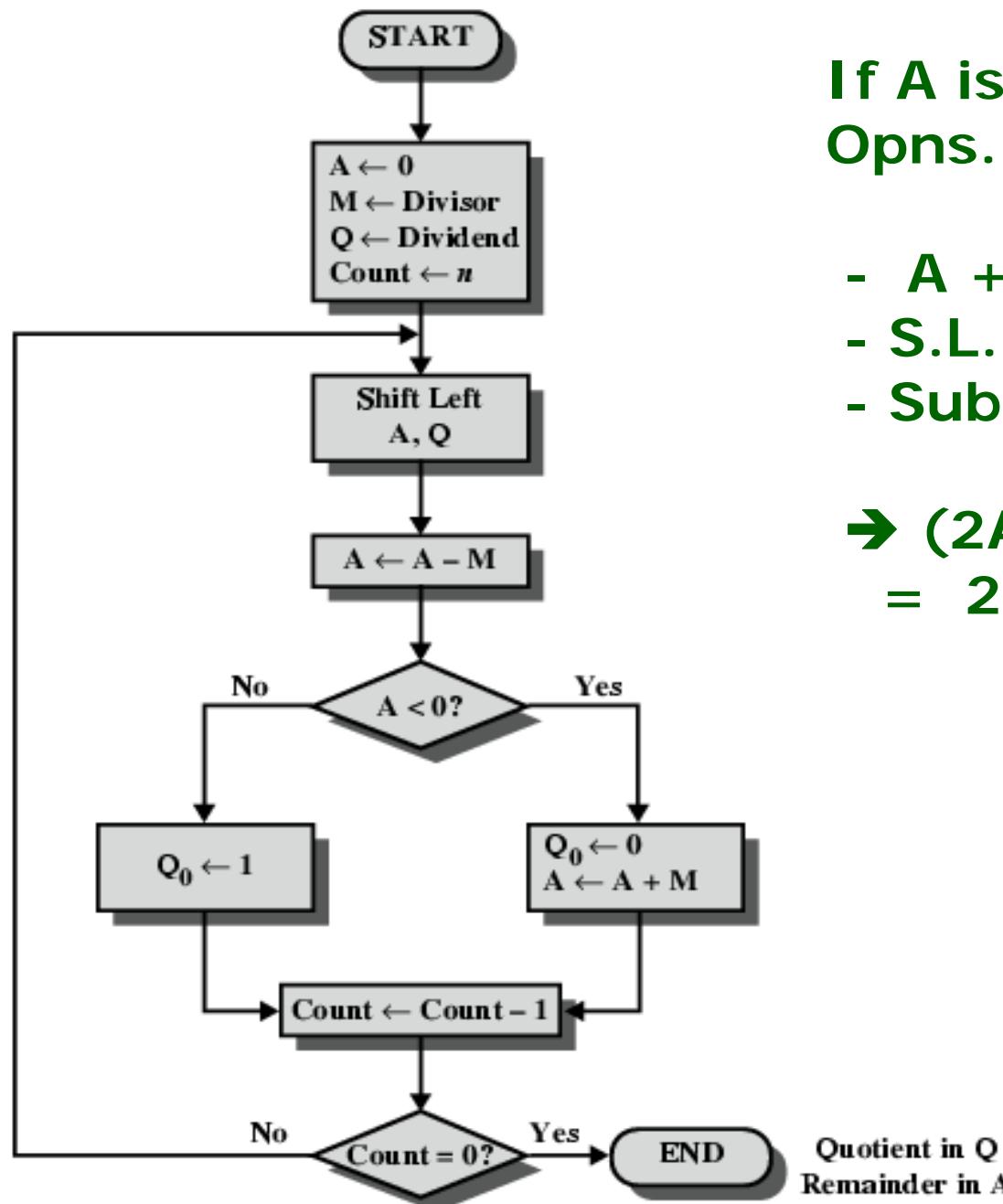

If A is -ve,
Opns. :

- $A + M$
- S.L. ($A+M$);
- Subtract M;

$$\begin{aligned}\rightarrow (2A + 2M) - M \\ = 2A + M\end{aligned}$$

Step 1: Repeat n times:

1. If $\text{sgn}(A) == 0$
 - Shift (left) A & Q (1-bit posn.)
 - $A = A - M;$
- else
 - Shift (left) A & Q (1-bit posn.)
 - $A = A + M;$

RESTORING DIVISION

2. If $\text{sgn}(A) == 0$

- o Set $Q_0 = 1;$
- o else $Q_0 = 0;$

Repeat n times:

- Shift (left) A & Q (1 bit posn.)
- $A = A - M;$
- If $\text{sgn}(A) == 1$ (-ve A)
 - o Set $Q_0 = 0;$
 - o $A = A + M;$

End

Step 2: If $\text{sgn}(A) == 1$

$A = A + M;$

NON RESTORING DIVISION

Else

- o Set $Q_0 = 1;$


End

Dividend,
Q = 1000;

Divisor,
M = 11.

- M =
11101

		OPN.	REG. A					REG. Q			
		INIT.	0	0	0	0	0	1	0	0	0
I	S. L.	0	0	0	0	1	0	0	0		
	SUB	1	1	1	1	0					
	Set Q ₀	1	1	1	1	0	0	0	0	0	0
II	S. L.	1	1	1	0	0	0	0	0	0	
	ADD	1	1	1	1	1					
	Set Q ₀	1	1	1	1	1	0	0	0	0	0
III	S. L.	1	1	1	1	0	0	0	0	0	
	ADD	0	0	0	0	1					
	Set-Q ₀	0	0	0	0	1	0	0	0	0	1
IV	S. L.	0	0	0	1	0	0	0	0	1	
	SUB	1	1	1	1	1					
	Set-Q ₀	1	1	1	1	1	0	0	1	0	
	ADD	0	0	0	1	0	0	0	1	0	
Final Result		0	0	0	1	0	0	0	1	0	
		REM					Q				

 

Floating Point Numbers

IEEE 32-bit single precision




IEEE 64-bit single precision

$$|E| = 11$$

$$|M| = 52$$

Density of Floating Point Numbers

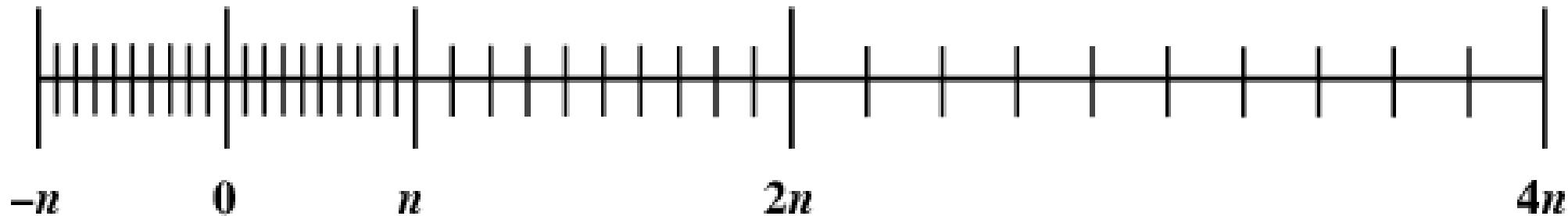

SEM Field

- ◆ Common case - signed-magnitude fraction
- ◆ Floating-point format - sign bit S , e bits of exponent E , m bits of unsigned fraction M ($m+e+1=n$)

S	Exponent E	Unsigned Significand M
-----	--------------	--------------------------

- ◆ Value of (S, E, M) : $F = (-1)^S \cdot M \cdot \beta^E$
 $((-1)^0 = 1 ; (-1)^1 = -1)$

- ◆ Maximal value - $M_{\max} = 1 - \text{ulp}$
- ◆ **ulp** - Unit in the last position - weight of the least-significant bit of the fractional significand
- ◆ Usually (not always) $\text{ulp} = 2^{-m}$

In IEEE 32-bit single precision;

E is a “signed exponent”, **E'** is in excess-127 Representation

$$E' = E + 127;$$

The end values are reserved for special use:

$$0 \leq E' \leq 255$$

$$1 \leq E' \leq 254; E = E' - 127;$$

$$-127 \leq E \leq 128;$$

$$-126 \leq E \leq 127;$$

**Range,
for Exponent:**

$$[2^{-126} \dots 2^{+127}] \Rightarrow 10^{\pm 38}$$

For Mantissa:

$$[2^{-23}] \Rightarrow 10^{-7}$$

In IEEE 64-bit single precision;

$$E' = E + 1023 ; 1 \leq E' \leq 2046$$

**Range,
for Exponent:**

$$[2^{-1022} \dots 2^{+1023}] \Rightarrow 10^{\pm 308}$$

For Mantissa:

$$[2^{-53}] \Rightarrow 10^{-16}$$

Floating-Point Formats of Three Machines

	IBM/370	DEC/VAX	Cyber 70
Word length (double)	32 (64) bits	32 (64) bits	60 bits
Significand+{hidden bit}	24 (56) bits	23 + 1 (55 + 1) bits	48 bits
Exponent	7 bits	8 bits	11 bits
Bias	64	128	1024
Base	16	2	2
Range of M	$\frac{1}{16} \leq M < 1$	$\frac{1}{2} \leq M < 1$	$1 \leq M < 2$
Representation of M	Signed-magnitude	Signed-magnitude	One's complement
Approximate range	$16^{63} \approx 7 \cdot 10^{75}$	$2^{127} \approx 1.9 \cdot 10^{38}$	$2^{1023} \approx 10^{307}$
Approximate resolution	$2^{-24} \approx 10^{-7} (10^{-17})$	$2^{-24} \approx 10^{-7} (10^{-17})$	$2^{-48} \approx 10^{-14}$

Binary Normalized Mantissa (IEEE):

1.<xxxx ..23 bits....xxxx>

0	10001000	.0010110
---	----------	-------------------------

Numerical Value (unnormalized): = +0.0010110.... x 2^9

0	10000101	.0110
---	----------	----------------------

Numerical Value (Normalized): = +1.0110.... x 2^6

1	00101000	.001010
---	----------	------------------------

Numerical Value (Normalized): = -1.001010.... x 2^{-87}

Special Values :

E' = 0 AND M = 0 → ZERO VALUE;

Both

± 0 and $\pm \infty$

E' = 255 AND M = 0 → INFINITY;

are possible

E' = 0 and M <> 0 → denormal numbers; $\pm 0.M \times 2^{-126}$

E' = 255 and M <> 0 → NaN; $0/0$; $\sqrt{-1}$

Exceptions :

Underflow, Overflow, Divide by zero and

Inexact → Result that requires rounding in order to be represented in one of the normal formats;

Invalid → 0/0 and sqrt(-1) are attempted.


Special values are set to the results.

Algms. For ADD/SUB, MULT/DIV, in normalized floating point opens.



ADD/SUB	MULT.	DIV.
<ul style="list-style-type: none">• Make smaller exp = large exp., by shifting opn.• Perform ADD/SUB on mantissas (get result with sign)	<ul style="list-style-type: none">• Add the E's and subtract 127• Mult. the Mantissas and get the sign	<ul style="list-style-type: none">• Subtract the E's and add 127• Div. The Mantissas and get the sign

**Normalize the result value, if necessary,
in all the three cases above.**


Floating point addition

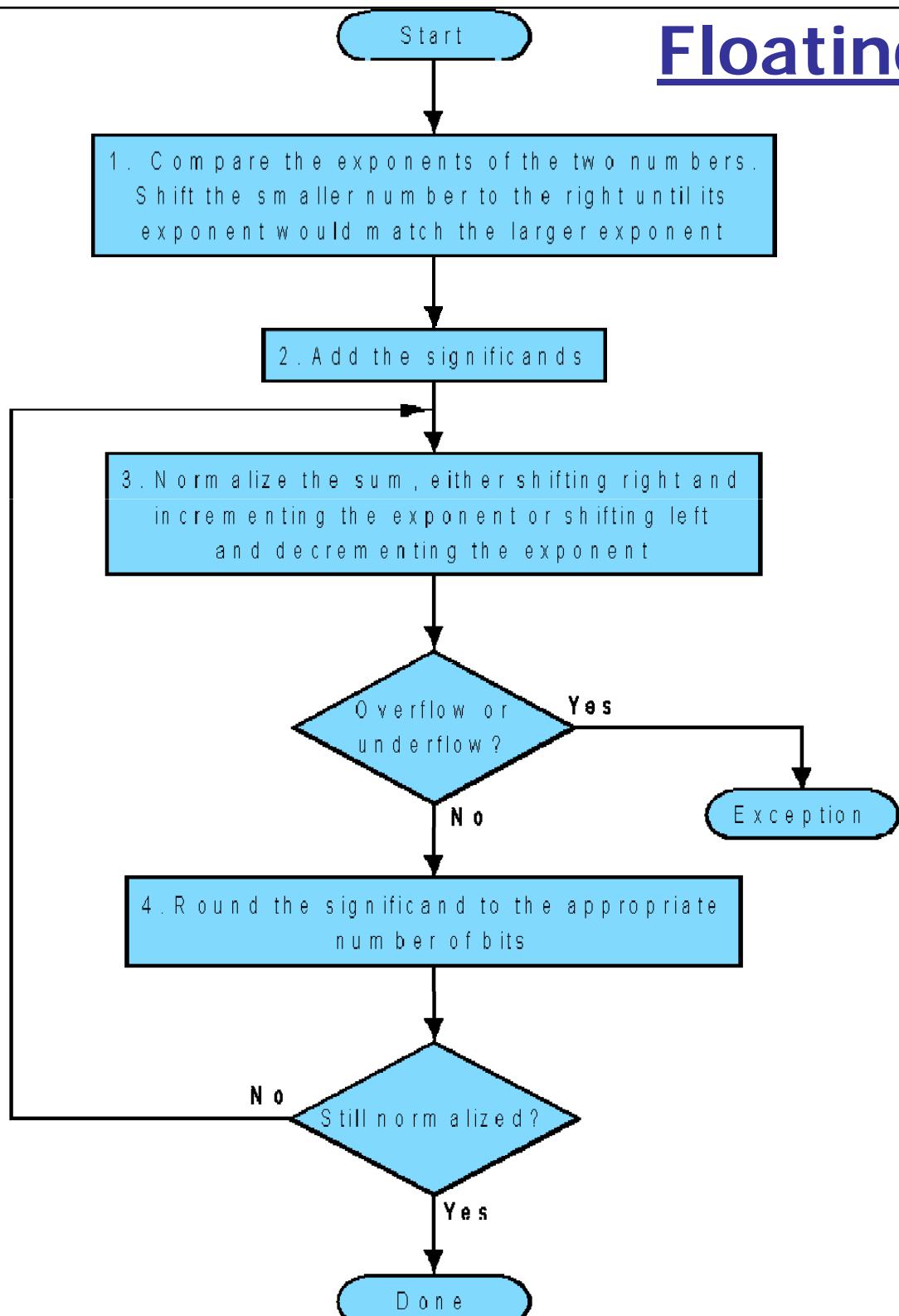


Floating point addition

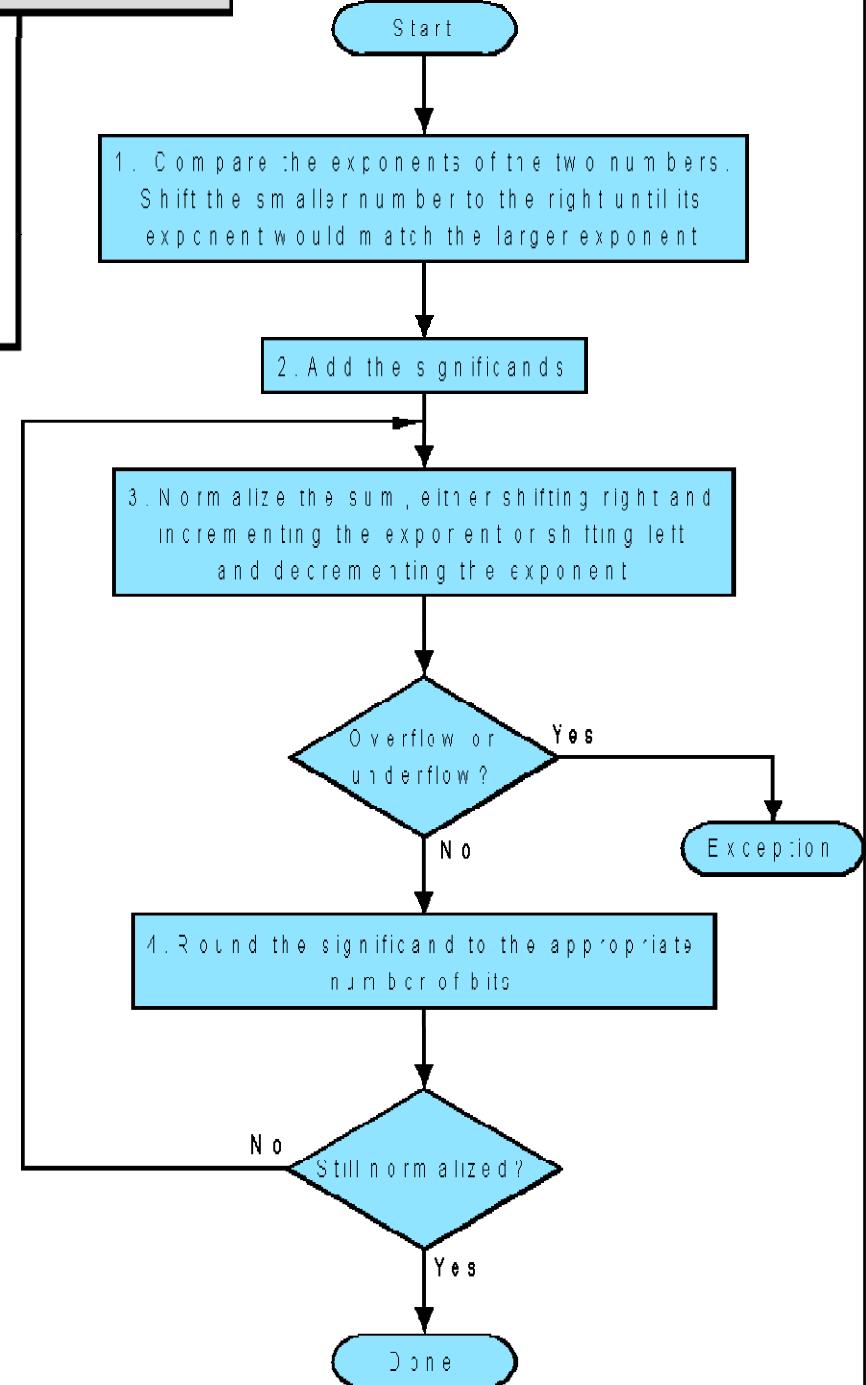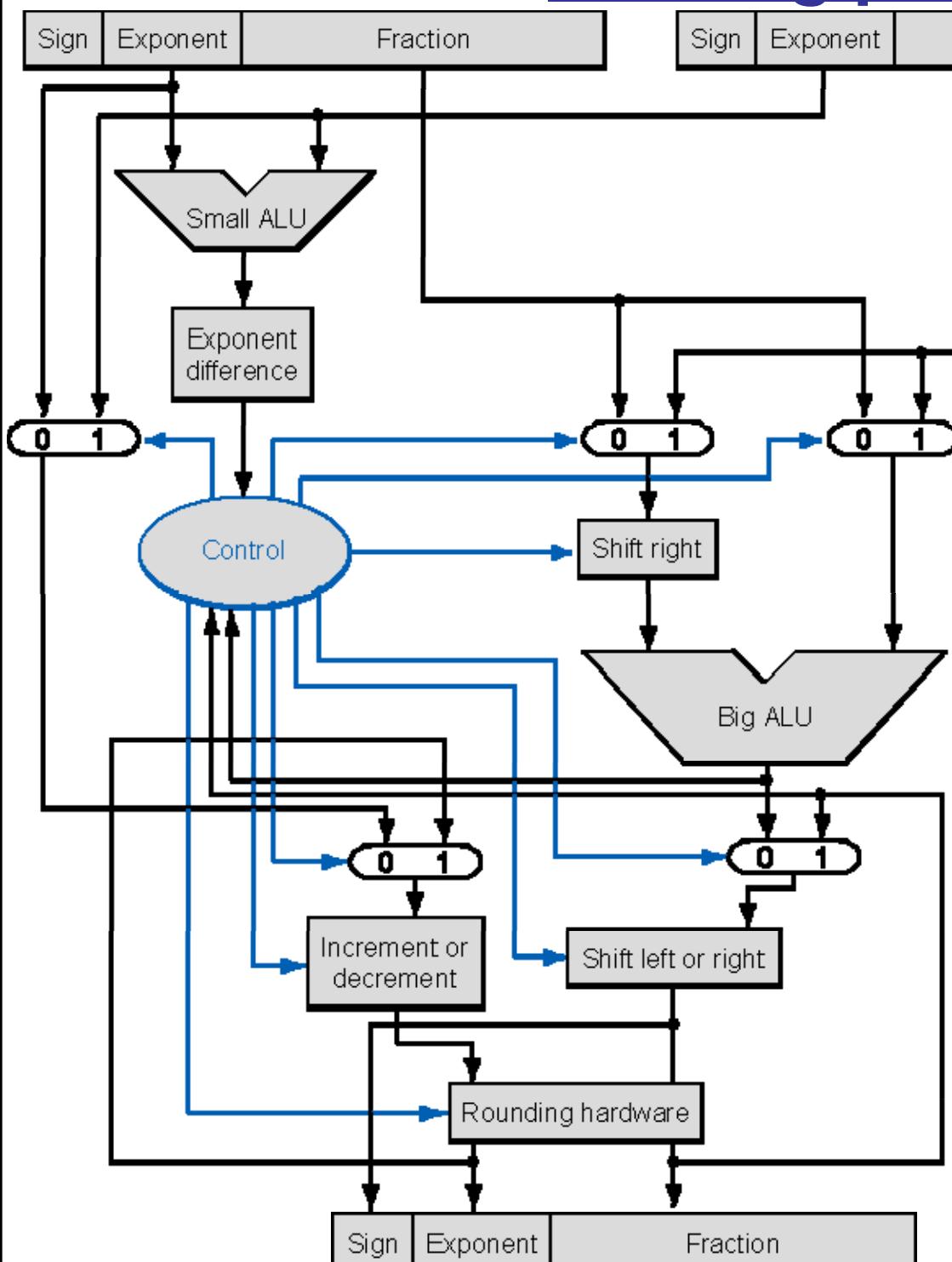


FP Addition & Subtraction Flowchart

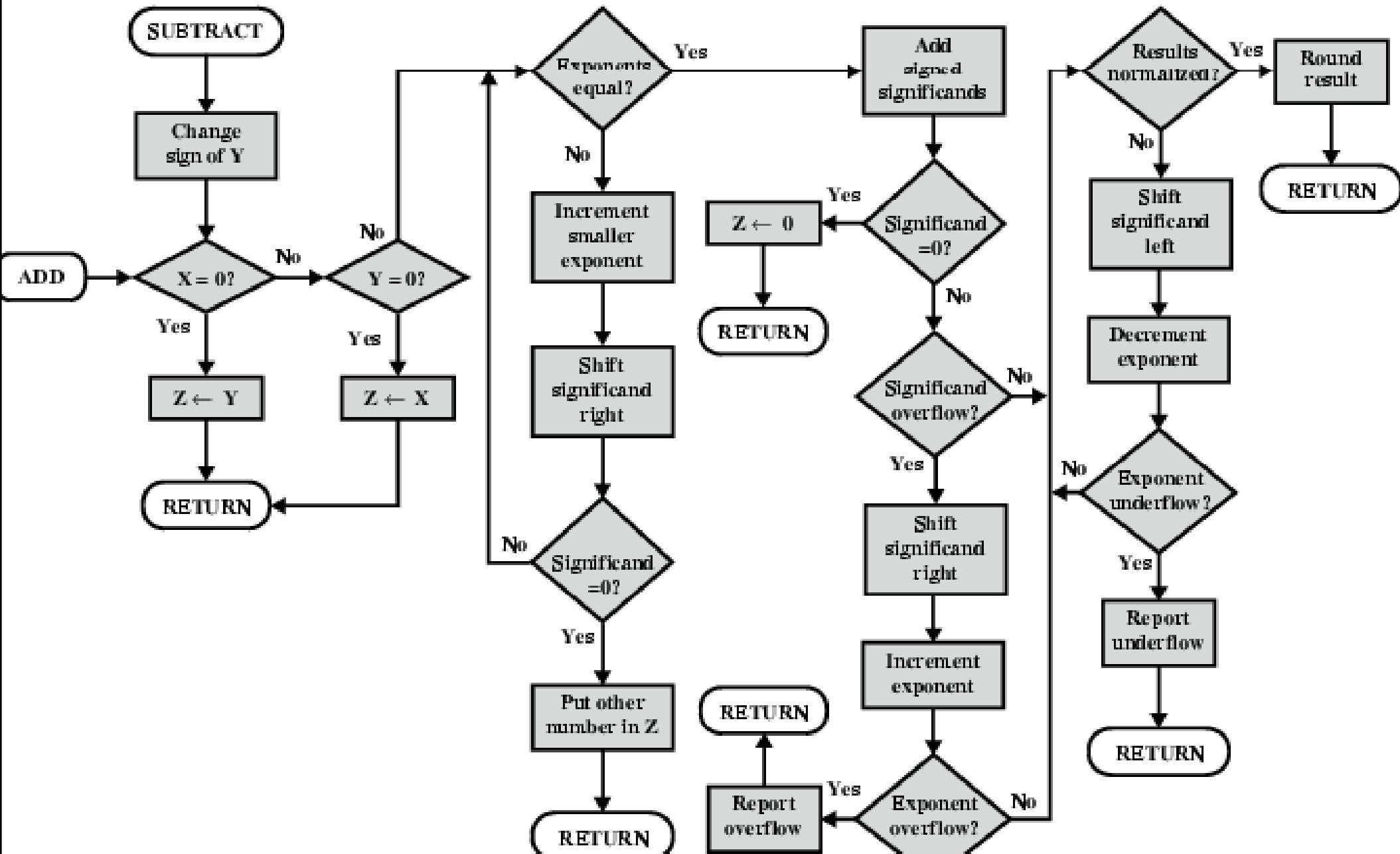

Circuitry for Addition/Subtraction

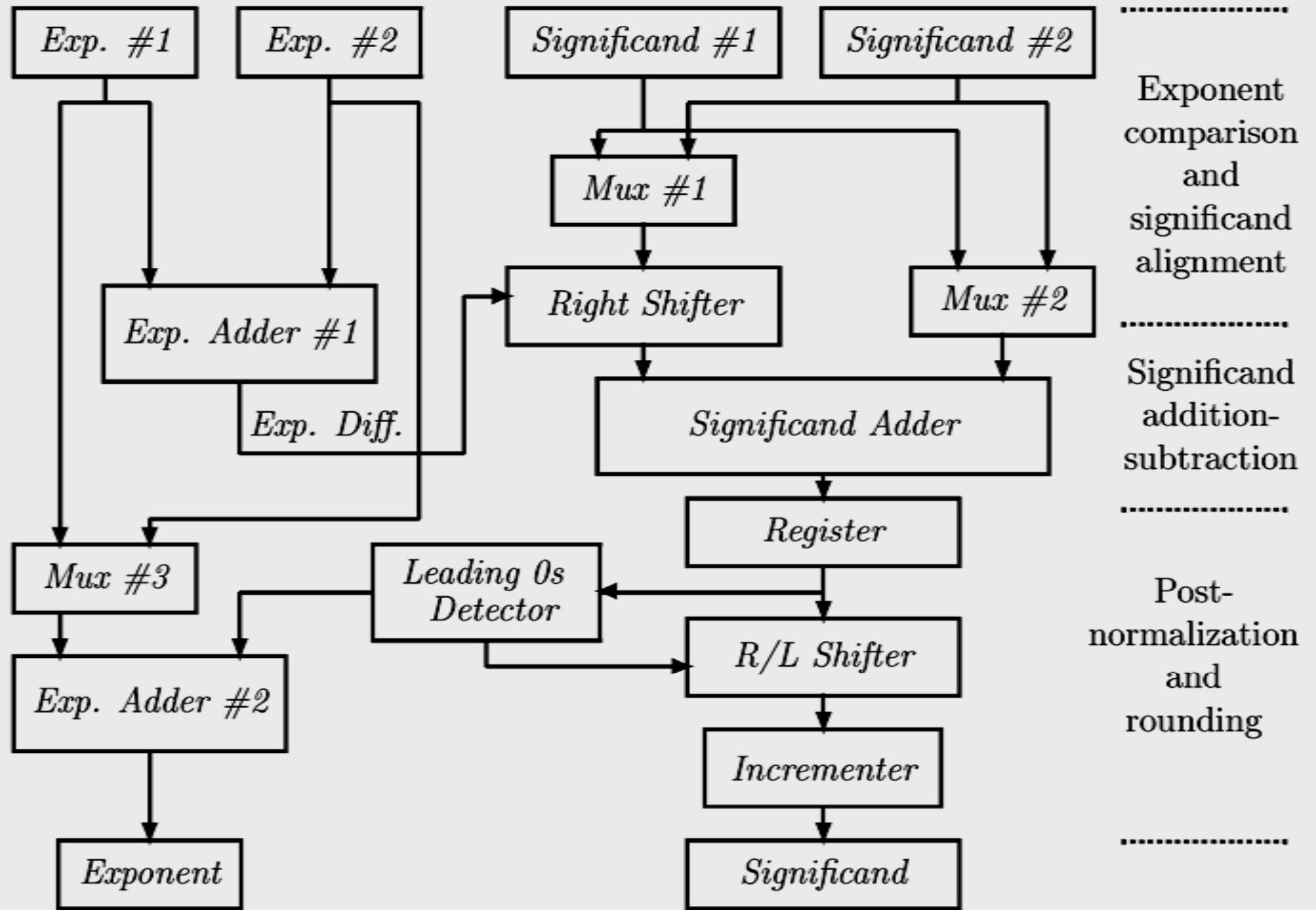

Floating Point Multiplication

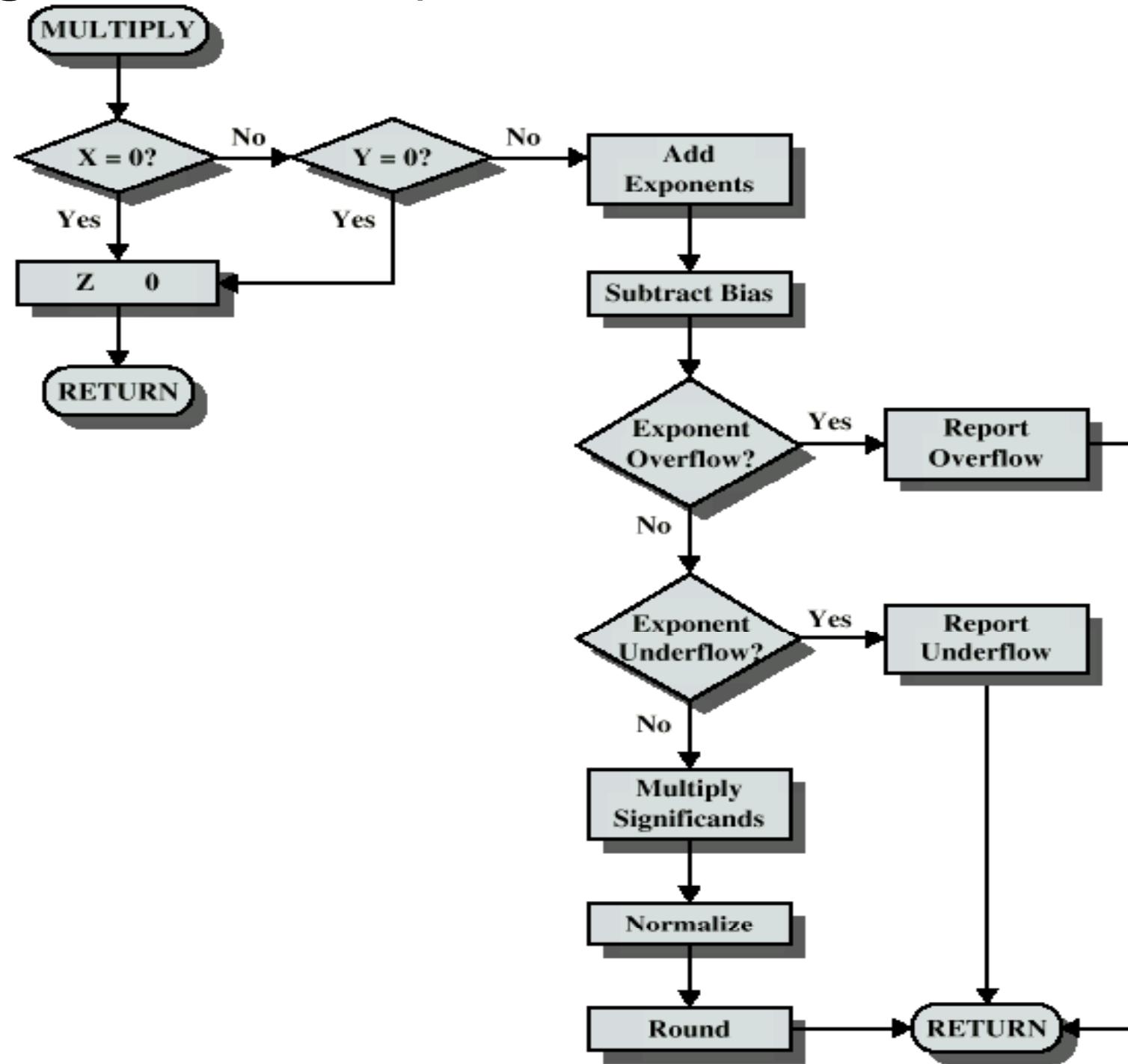

Floating Point Division

